

Digital Electronics 2: Experiment Verilog

Laboratory Book

Omar Sharif, *EIE Undergraduate*

Raphael Bijaoui, *EIE Undergraduate*

EEE Department, Imperial College


Experiment 1: Schematic capture using Quartus 7-segment display

Sunday, December 8, 2019

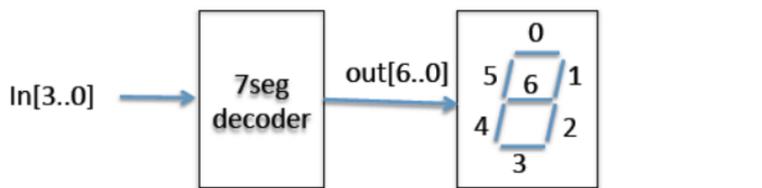1:48 PM

In Experiment 1, we were tasked with designing a 7-segment decoder using 'schematic-entry' method (as opposed to using Verilog).


The decoder output out[6:0] drives the 7 segments on the HEX displays. The LED segments are low active which means that the LED will light up (ON) only if the corresponding digital signal is 0V.




in[3..0]	out[6:0]	Digit	in[3..0]	out[6:0]	Digit
0000	1000000	0	1000	0000000	8
0001	1111001	1	1001	0010000	9
0010	0100100	2	1010	0001000	A
0011	0110000	3	1011	0000011	b
0100	0011001	4	1100	1000110	C
0101	0010010	5	1101	0100001	d
0110	0000010	6	1110	0000110	E
0111	1111000	7	1111	0001110	F


Using the truth table, it is possible to use K-maps to minimize the logic required for the decoder – however Quartus performs the logic minimization and is better taking into account the architecture of the FPGA chip than us!

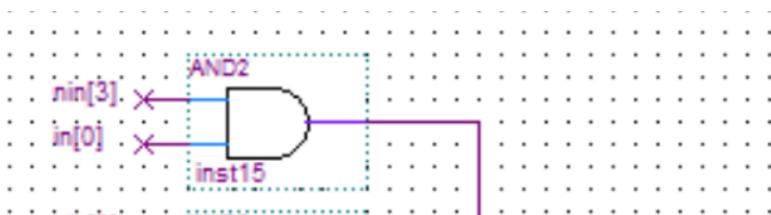We therefore downloaded the incomplete 7 segment decoder circuit and implemented the equation $\text{out4} = \text{/in3*in0} + \text{/in3*in2*}/\text{in1} + \text{/in2*}/\text{in1*in0}$ using the schematic editor (as shown below) to complete the design.



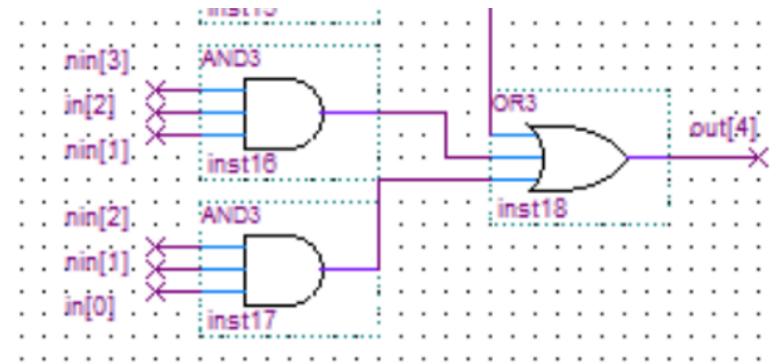

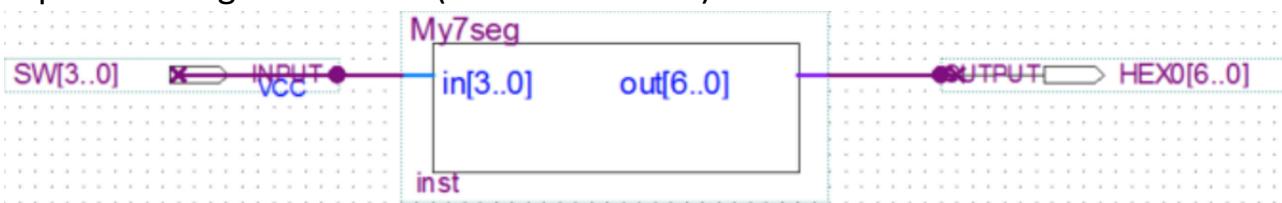We then encapsulated the circuit into a module (entity), setting this module as the top-level design schematic (as shown below).



To run the module, we need to associate the design with the physical pins of the Cyclone V FPGA board. The top level input/output pins are shown as a list below and the I/O standard (i.e. interface voltages) were set "3.3V LVTTL".

Signal Name	Pin Location
HEX0[6]	PIN_AH28
HEX0[5]	PIN_AG28
HEX0[4]	PIN_AF28
HEX0[3]	PIN_AG27
HEX0[2]	PIN_AE28
HEX0[1]	PIN_AE27
HEX0[0]	PIN_AE26
SW[3]	PIN_AF10
SW[2]	PIN_AF9
SW[1]	PIN_AC12
SW[0]	PIN_AB12

We then examined how the propagation delay from inputs to outputs varies with temperature for (Slow 1100mV) with

- RR (CLK rising - Output rising)
- RF (CLK rising - Output falling)
- FR (CLK falling - Output rising)
- FF (CLK falling - Output falling)

Slow Model is the worst case delay & Fast is the best case delay

0 Degree Model (ns)

Propagation Delay						
	Input Port	Output Port	RR	RF	FR	FF
1	SW[0]	HEX0[0]	8.320	8.547	8.579	8.814
2	SW[0]	HEX0[1]	8.520	8.946	8.779	9.259
3	SW[0]	HEX0[2]		8.825	8.795	
4	SW[0]	HEX0[3]	7.964	8.141	8.219	8.450
5	SW[0]	HEX0[4]	8.737			9.388
6	SW[0]	HEX0[5]	8.622			9.394
7	SW[0]	HEX0[6]	8.060	8.155	8.318	8.421
8	SW[1]	HEX0[0]	7.978	8.226	8.267	8.497
9	SW[1]	HEX0[1]	8.273	8.648	8.568	8.920
10	SW[1]	HEX0[2]	8.186			8.771
11	SW[1]	HEX0[3]	7.761	7.887	8.059	8.162
12	SW[1]	HEX0[4]		8.800	8.684	
13	SW[1]	HEX0[5]	8.381	8.790	8.677	9.063
14	SW[1]	HEX0[6]	7.718	7.834	8.007	8.105
15	SW[2]	HEX0[0]	8.520	8.822	8.800	9.155
16	SW[2]	HEX0[1]	8.995			9.636
17	SW[2]	HEX0[2]	8.740	9.106	9.020	9.439
18	SW[2]	HEX0[3]	8.436	8.539	8.716	8.827
19	SW[2]	HEX0[4]	8.937	9.396	9.217	9.729
20	SW[2]	HEX0[5]	9.097	9.483	9.377	9.771
21	SW[2]	HEX0[6]	8.260	8.430	8.540	8.763
22	SW[3]	HEX0[0]	8.128	8.417	8.344	8.581
23	SW[3]	HEX0[1]	8.423	8.846	8.784	9.124
24	SW[3]	HEX0[2]	8.356	8.709	8.573	8.874
25	SW[3]	HEX0[3]	7.863	8.037	8.224	8.315
26	SW[3]	HEX0[4]		8.997	8.767	
27	SW[3]	HEX0[5]	8.524	8.981	8.885	9.259
28	SW[3]	HEX0[6]	7.864	8.021	8.081	8.186

85 Degree Model (ns)

Propagation Delay						
	Input Port	Output Port	RR	RF	FR	FF
1	SW[0]	HEX0[0]	8.716	8.921	8.901	9.112
2	SW[0]	HEX0[1]	8.980	9.365	9.173	9.592
3	SW[0]	HEX0[2]		9.247	9.163	
4	SW[0]	HEX0[3]	8.371	8.506	8.563	8.732
5	SW[0]	HEX0[4]	9.167			9.721
6	SW[0]	HEX0[5]	9.072			9.726

7	SW[0]	HEX0[6]	8.446	8.510	8.632	8.702
8	SW[1]	HEX0[0]	8.389	8.609	8.620	8.826
9	SW[1]	HEX0[1]	8.722	9.060	8.954	9.273
10	SW[1]	HEX0[2]	8.643			9.147
11	SW[1]	HEX0[3]	8.166	8.254	8.402	8.472
12	SW[1]	HEX0[4]		9.218	9.072	
13	SW[1]	HEX0[5]	8.821	9.202	9.054	9.417
14	SW[1]	HEX0[6]	8.120	8.199	8.352	8.417
15	SW[2]	HEX0[0]	8.969	9.238	9.172	9.474
16	SW[2]	HEX0[1]	9.463			9.988
17	SW[2]	HEX0[2]	9.235	9.570	9.438	9.806
18	SW[2]	HEX0[3]	8.851	8.923	9.049	9.126
19	SW[2]	HEX0[4]	9.420	9.846	9.623	10.082
20	SW[2]	HEX0[5]	9.554	9.919	9.753	10.123
21	SW[2]	HEX0[6]	8.700	8.828	8.902	9.063
22	SW[3]	HEX0[0]	8.580	8.835	8.718	8.923
23	SW[3]	HEX0[1]	8.918	9.298	9.196	9.500
24	SW[3]	HEX0[2]	8.855	9.176	8.995	9.266
25	SW[3]	HEX0[3]	8.305	8.435	8.583	8.637
26	SW[3]	HEX0[4]		9.450	9.176	
27	SW[3]	HEX0[5]	9.010	9.433	9.287	9.634
28	SW[3]	HEX0[6]	8.306	8.420	8.445	8.509

RR & FF gaps vs. RF & FR gaps -> these are representative of the cases when there a RF in the input never causes a FR in the output

We got 2 key takeaways from this experiment:

1. the **0 degree model had lower propagation times than the 85 degree model.**
This can be explained because at lower temperatures there is less resistance in the wires within the FPGA. The effect of increased heat on the atomic structure of a wire to make the atoms vibrate, making it more difficult for signals to propagate.
2. It was very tedious to make the block diagram! The need for code clarity is real.

Resources

Finally, we examined the compilation report for our resources used. We found that this design used only 4 out of 32,060 ALMs (Adaptive Logic Modules), 11 of the 457 I/O pins and none of the other resources.

Logic utilization (in ALMs)	4 / 32,070 (< 1 %)
Total registers	0
Total pins	11 / 457 (2 %)

Experiment 2: 7-segment Decoder in Verilog HDL


Sunday, December 8, 2019 1:49 PM

We found the process of designing the 7-segment decoder using schematic design to be limiting and time consuming. In reality designers would use a hardware description language to specify design.

For Experiment 2, we designed a module for the 7-segment decoder

```
module hex_to_7seg (out,in);
    output [6:0] out; // low-active out
    input [3:0] in; // 4-bit binary inp
    reg [6:0] out; // make out a varia

    always @ (*)
        case (in)
            4'h0: out = 7'b1000000;
            4'h1: out = 7'b1111001;
            4'h2: out = 7'b0100100;
            4'h3: out = 7'b0110000;
            4'h4: out = 7'b0011001;
            4'h5: out = 7'b0010010;
            4'h6: out = 7'b0000010;
            4'h7: out = 7'b1111000;
            4'h8: out = 7'b0000000;
            4'h9: out = 7'b0011000;
            4'ha: out = 7'b0001000;
            4'hb: out = 7'b0000011;
            4'hc: out = 7'b1000110;
            4'hd: out = 7'b0100001;
            4'he: out = 7'b0000110;
            4'hf: out = 7'b0001110;
        endcase
endmodule
```

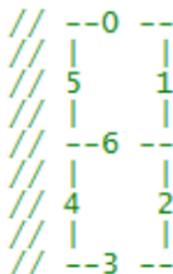

We then specified the top-level design module in Verilog - analogous to encapsulating our schematic design in Experiment 1.

```
module ex2_top (
    SW, // input switches
    HEX0 // Hex output on 7 segment display
);
    input [3:0] SW; // declare input/output ports
    output [6:0] HEX0;

    hex_to_7seg SEG0 (HEX0, SW);

endmodule
```

PIN ASSIGNMENT

In Experiment 1, we used the pin assignment editor to associate pins – this is also tedious. Instead we used the generated qsf file along with the provided pin_assignment.txt to assign pins. In the qsf file we find the following statements:

```
set_instance_assignment -name IO_STANDARD "3.3-V LVTTL" -to HEX0[4]
set_location_assignment PIN_AF28 -to HEX0[4]
```

1. The first line defines the voltage standard used by the HEX0[4] signal (3.3V logic).
2. The second line defines the physical pin location of HEX0[4] is PIN_AF28.

Experiment 3: 10-bit binary switch values on three 7-segment displays

Sunday, December 8, 2019 1:50 PM

In Experiment 3, we were tasked to create our own design to display all 10-bit sliding switches as hexadecimal values on three 7 segment LED displays. Our top module is shown below:

```
1  module ex3_top(
2    SW,
3    HEX0, HEX1, HEX2
4  );
5
6    input [9:0] SW;
7    output [6:0] HEX0;
8    output [6:0] HEX1;
9    output [6:0] HEX2;
10
11   hex_to_7seg SEG0(HEX0,SW[3:0]);
12   hex_to_7seg SEG1(HEX1,SW[7:4]);
13   hex_to_7seg SEG2(HEX2,SW[9:8]);
14
15 endmodule
```


1. This code in the top-level specification for 10-bit binary switch values on three 7-segment displays
2. It takes as input the 10 switch value (0 -> off & 1 -> on).
3. This is then relayed into three hex_to_7seg function calls, each taking as input the required switch values.
4. These values are specified using SW[3:0] which takes SW0, SW1, SW2, etc.
5. Since there are only 2 switches SW[9:8] specifying one hex values, we have the maximum values as being **10'h03FFFFFF**

Experiment 4 (Optional): Displaying 10-bit binary as displays


Sunday, December 8, 2019 1:50 PM


In Experiment 4, we were tasked to build upon our own design to display all 10-bit sliding windows.

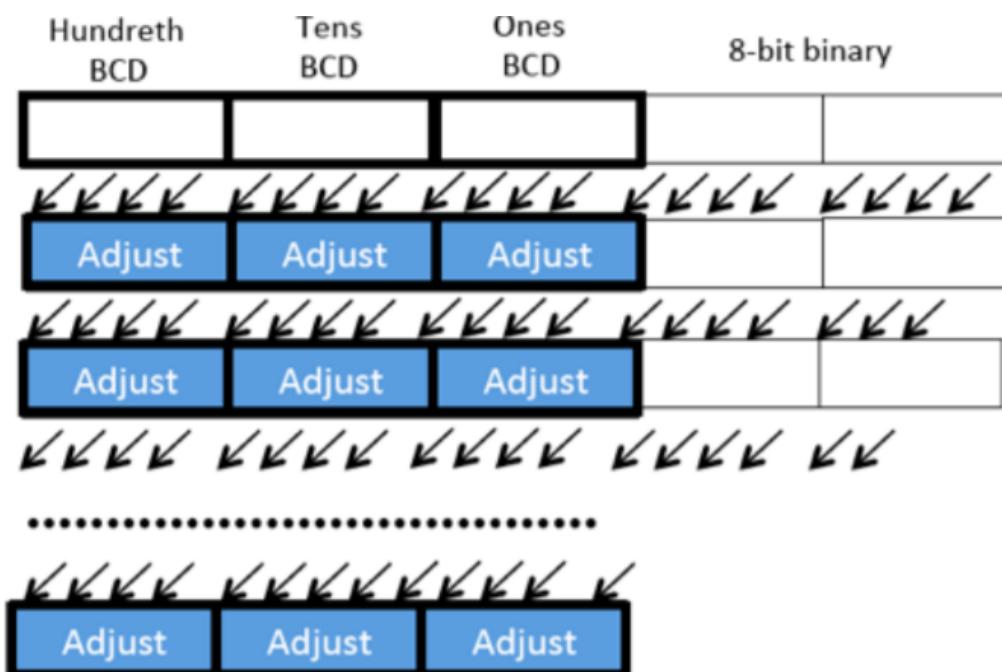To do this, we started off with the "Shift and Add 3" Algorithm which was presented to us in class. By applying all the arithmetic/logic blindly we took the wiring approach to perform the binary to BCD conversion. The shifting in hardware is simple. It does not require gates, only connecting signals with one bit at a time.




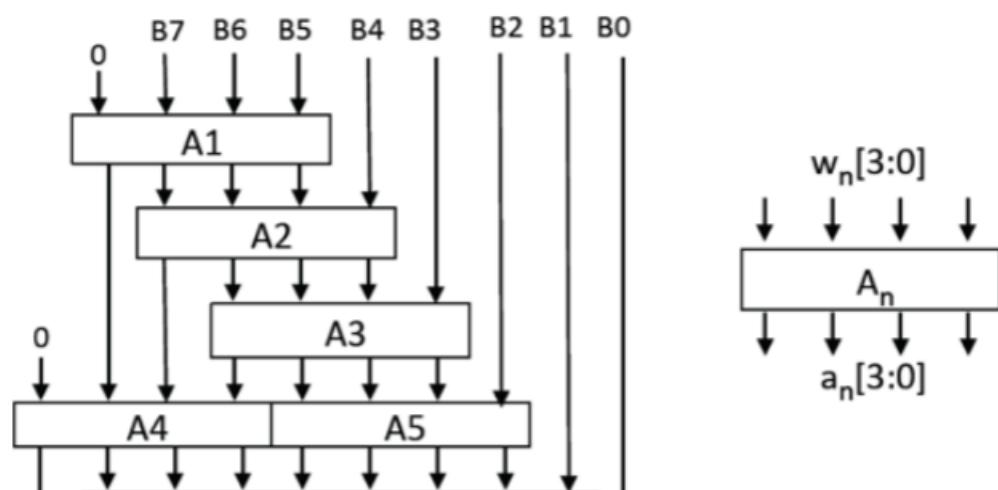Using the example given to us in Lecture 10 for an 8 bit converter, we used the same principle of bit propagation of binary bits into the system to isolate where the add3_ge5 modules will be used.



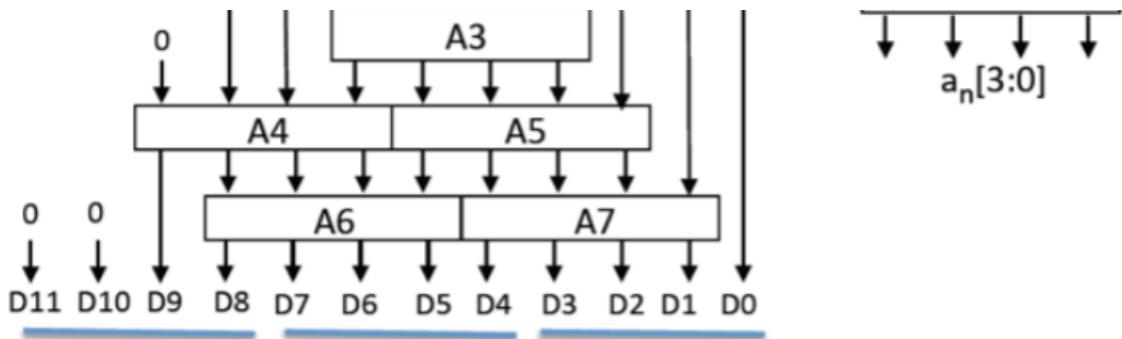

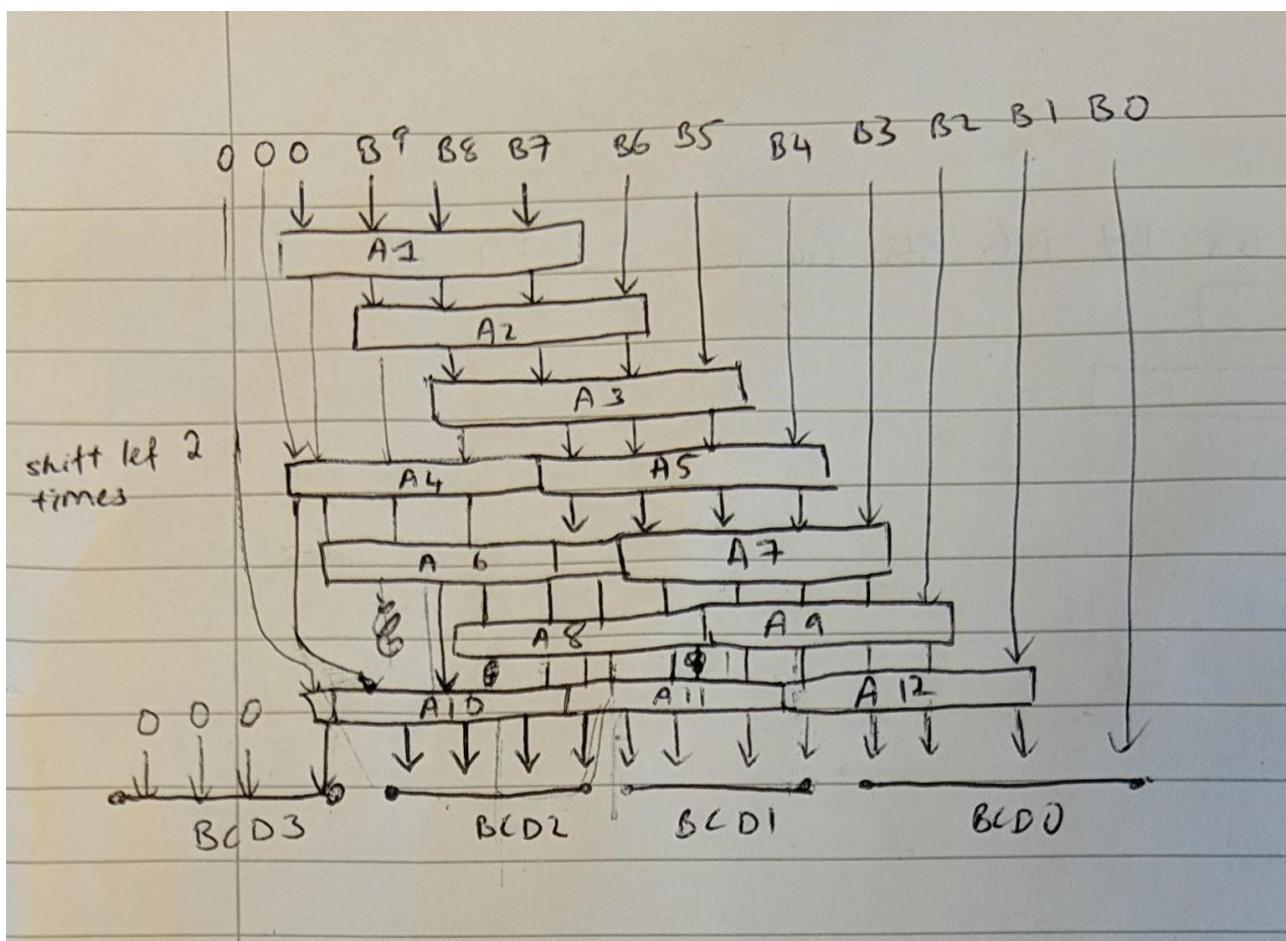Below it the diagram we constructed to help us to design the module.



We then specified our top level design module passing the converted BCD values as wires into our hex_to_7seg modules to output our results in 4 displays. Our top-level design module can be seen below:

```
module ex4_top(SW, HEX0, HEX1, HEX2, HEX3);
    input [9:0] SW;
    output [6:0] HEX0;
    output [6:0] HEX1;
    output [6:0] HEX2;
    output [6:0] HEX3;
```

```

wire [3:0] BCD_0, BCD_1, BCD_2, BCD_3;

binary_to_bcd_10 bin2bcd10(sw, BCD_0, BCD_1, BCD_2, BCD_3);

hex_to_7seg SEG0(HEX0, BCD_0);
hex_to_7seg SEG1(HEX1, BCD_1);
hex_to_7seg SEG2(HEX2, BCD_2);
hex_to_7seg SEG3(HEX3, BCD_3);

endmodule


```


Wiring up of the binary to bcd

```

8 //-----
9 // For more explanation of how this work, see
10 // ... instructions on www.ee.ic.ac.uk/pcheung/teaching/E2_experiment
11
12 module binary_to_bcd_10 (B, BCD_0, BCD_1, BCD_2, BCD_3);
13
14     input [9:0] B;      // binary input number
15     output [3:0] BCD_0, BCD_1, BCD_2, BCD_3;    // BCD digit LSD to MSD
16
17     wire [3:0] w1,w2,w3,w4,w5,w6,w7,w8,w9,w10,w11,w12; //Check how many wires needed- do diagram
18     wire [3:0] a1,a2,a3,a4,a5,a6,a7,a8,a9,a10,a11,a12;
19
20     // Instantiate a tree of add3-if-greater than or equal to 5 cells
21     // ... input is w_n, and output is a_n
22     add3_ge5 A1 (w1,a1);
23     add3_ge5 A2 (w2,a2);
24     add3_ge5 A3 (w3,a3);
25     add3_ge5 A4 (w4,a4);
26     add3_ge5 A5 (w5,a5);
27     add3_ge5 A6 (w6,a6);
28     add3_ge5 A7 (w7,a7);
29     add3_ge5 A8 (w8,a8);
30     add3_ge5 A9 (w9,a9);
31     add3_ge5 A10 (w10,a10);
32     add3_ge5 A11 (w11,a11);
33     add3_ge5 A12 (w12,a12);
34
35     // wire the tree of add3 modules together
36     assign w1 = {1'b0, B[9:7]}; // w1 is the input port to module A1
37     assign w2 = {a1[2:0], B[6]};
38     assign w3 = {a2[2:0], B[5]};
39     assign w4 = {1'b0, a1[3], a2[3], a3[3]};
40     assign w5 = {a3[2:0], B[4]};
41     assign w6 = {a4[2:0], a5[3]};
42     assign w7 = {a5[2:0], B[3]};
43     assign w8 = {a6[2:0], a7[3]};
44     assign w9 = {a7[2:0], B[2]};
45     assign w10 = {1'b0, a4[3], a6[3], a8[3]};
46     assign w11 = {a8[2:0], a9[3]};
47     assign w12 = {a9[2:0], B[1]};
48
49
50     // connect up to four BCD digit outputs
51     assign BCD_0 = {a12[2:0], B[0]};
52     assign BCD_1 = {a11[2:0], a12[3]};
53     assign BCD_2 = {a10[2:0], a11[3]};
54     assign BCD_3 = {1'b0, a10[3]};
55
56 endmodule
57

```

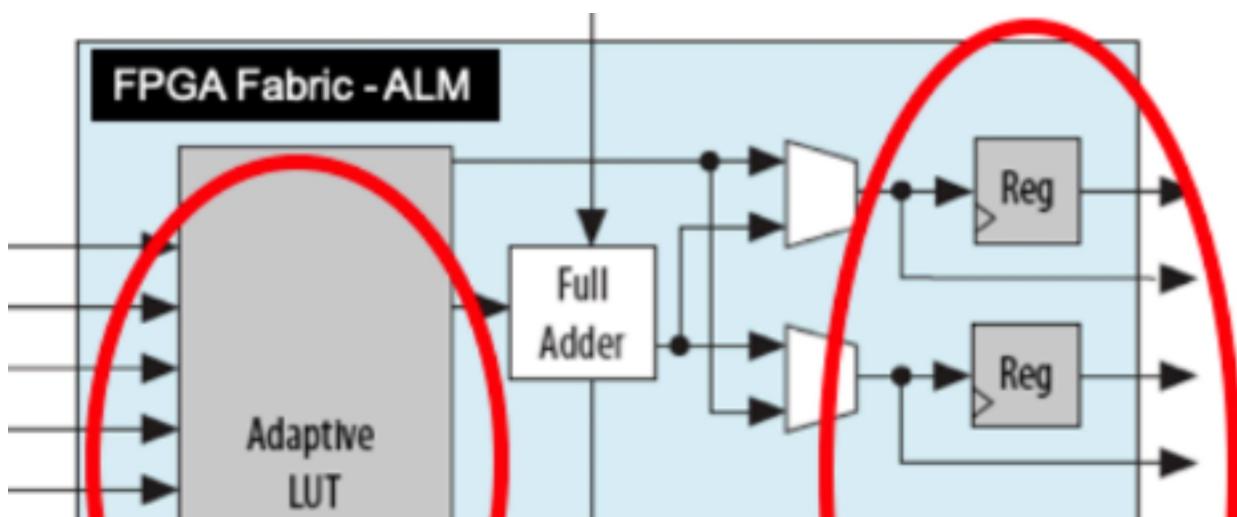

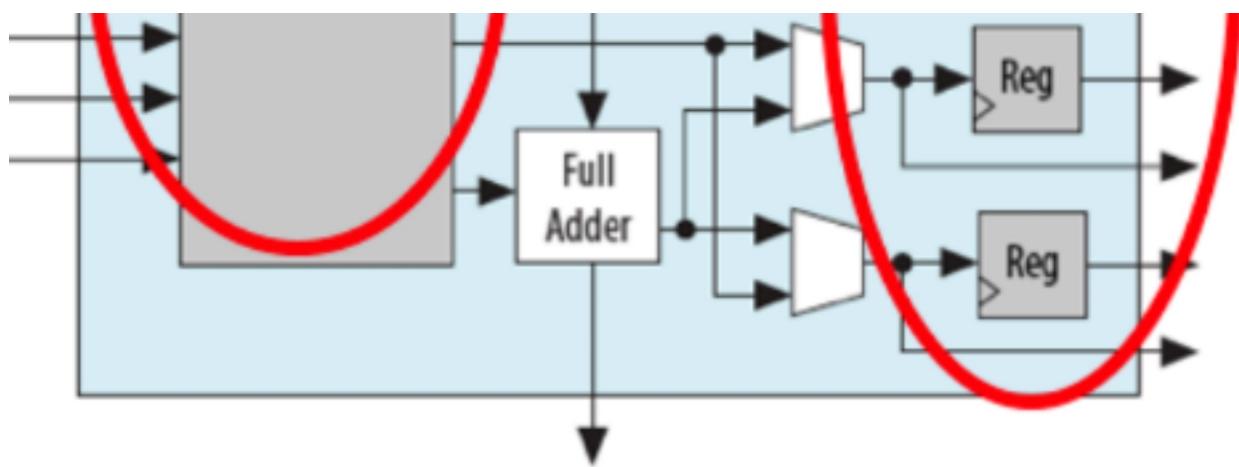

Experiment 5: Counters & FSMs

Sunday, December 8, 2019 1:51 PM

In Experiment 5, we were tasked with designing an 8-bit counter as shown below:

```
'timescale 1ns / 100ps

module counter_8(
    clock,
    enable,
    count
);

parameter BIT_SZ = 8;
input clock;
input enable;
output [BIT_SZ-1:0] count;


reg [BIT_SZ-1:0] count;
initial count = 0;


always @ (posedge clock)
    if (enable == 1'b1)
        count <= count + 1'b1;

endmodule
```

After we ensured our design was correct, we looked to simulate our design using the **Modelsim** environment. In the transcript window we ran the commands to add the *clock* and *count* signals as waveforms (showing count as hexadecimal) before driving the clock with a 50MHz signal and running the simulator for 5 clock cycles.

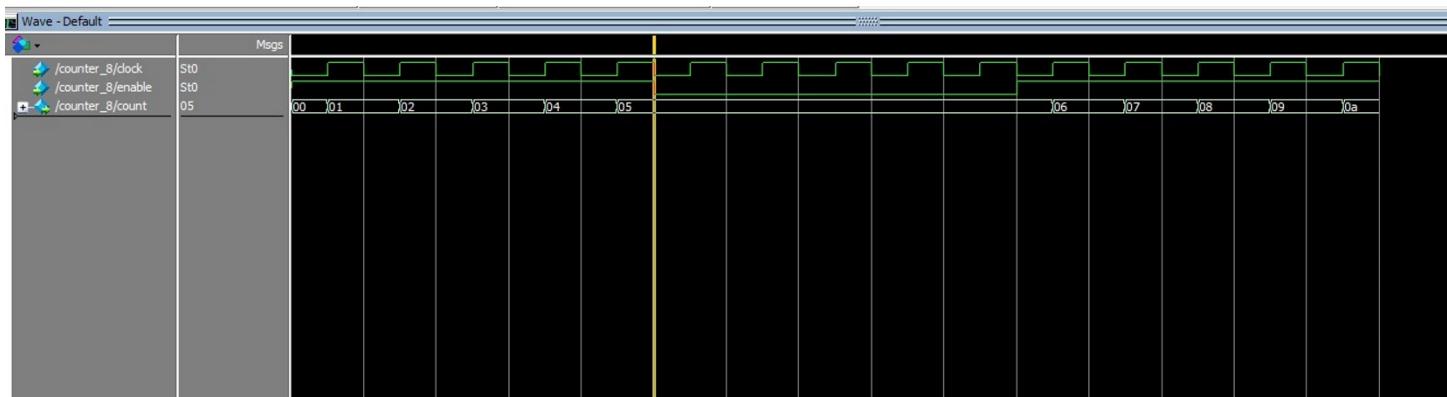The timing-diagram below was created using sequential instructions.



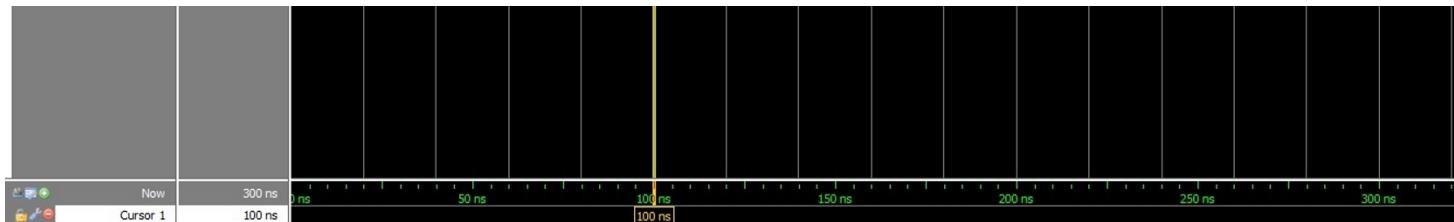

We then created a do-file to run as a testbench and simulate our design:

DO-file

```
add wave clock enable  
add wave -hexadecimal count  
force clock 0 0, 1 10ns -repeat 20ns  
force enable 1  
run 100ns  
force enable 0  
run 100ns  
force enable 1  
run 100ns
```

Experiment 6: Implementing a 16-bit counter on L

Sunday, December 8, 2019 1:52 PM

In Experiment 6, we were tasked with building a 16-bit Cascade Counter having previously standard 16-bit counter, The problem here was that counter was moving at 20MHz which observe the changes. A divide-by-50000 circuit was needed to generate a 1 cycle high pulse the output signal tick provides one enable pulse every millisecond

COUNTER

To build these, the first step was to extend our 8 bit counter to allow it to count to 16 bits [BIT_SZ-1:0], we simply set BIT_SZ = 16 in our code from Experiment 5. Then we wired the hex_to_7seg modules

Compilation Report

Frequency

After compiling the design, we investigated the *maximum* frequencies of the project at different

Slow 1100mV OC Model Fmax Summary				
<input type="button" value="Filter"/> <<Filter>>				
	Fmax	Restricted Fmax	Clock Name	Note
1	438.02 MHz	438.02 MHz	CLOCK_50	

Slow 1100mV 85C Model Fmax Summary				
<input type="button" value="Filter"/> <<Filter>>				
	Fmax	Restricted Fmax	Clock Name	Note
1	460.19 MHz	460.19 MHz	CLOCK_50	

Here, the Fmax for a higher temperature is higher than the Fmax for a lower temperature learnt in Exercise 1, where we expected the opposite to happen as things got hotter.

We found out that there are 2 factors that affect the Fmax. One is the Resistance of the circuit causing the overall electron mobility to decrease. Another is the threshold voltage which also varies with temperature.

temperature- this goes against what we learnt in Exercise 1, where we expected the opposite to happen as things got hotter.

We found out that there are 2 factors that affect the Fmax. One is the Resistance of the circuit which will increase with temperature causing the overall electron mobility to decrease. Another is the threshold voltage of the transistor which also varies with temperature.

In this case, we can say that the overall effect of the threshold voltage difference between the 2 temperatures had a greater effect on the Fmax than the increase in resistance which leads to these results.

We could also see our slack times for both Setup and Hold:

SETUP

Slow 1100mV 0C Model Setup Summary



	Clock	Slack	End Point TNS
1	CLOCK_50	-1.283	-15.305

Slow 1100mV 85C Model Setup Summary



	Clock	Slack	End Point TNS
1	CLOCK_50	-1.173	-14.055

HOLD

Slow 1100mV 0C Model Hold Summary



	Clock	Slack	End Point TNS
1	CLOCK_50	0.369	0.000

Slow 1100mV 85C Model Hold Summary



	Clock	Slack	End Point TNS
1	CLOCK_50	0.367	0.000

All of our slack times are non-zero, which shows there is some form of bottleneck in our system.

Our negative slack shows that we have not met the timing constraints given by Quartus for our given design.

To fix this, we could either relax the constraints set up, or come up with another design with a better functionality to meet the constraints.

Our hold time shows that the signal can get from the startpoint to the endpoint of the timing path fast enough for the circuit to operate correctly. It is the difference between the required time and the arrival time for the timing path.

To calculate the maximum frequency, we use the equation:

$$F_{max} = 1 / (t\{c-q\} + t\{p\} + t\{setup\})$$

$t\{c-q\}$ = is delay from the 'clock' to the output Q

$t\{p\}$ = is the propagation delay for device X


$t\{setup\}$ = is the setup time

Timing Analyzer

- SETUP - DATA must reach its new value at least **ts (setup slack)** before the positive edge of the clock: **$ts = required\ time - arrival\ time$**
- HOLD – DATA must be held constant for at least **th (hold time)** after the positive edge of the clock: **$th = arrival\ time - required\ time$**

(note, the setup and hold times are measured with respect to the active clock edge only)

CASCADE COUNTER

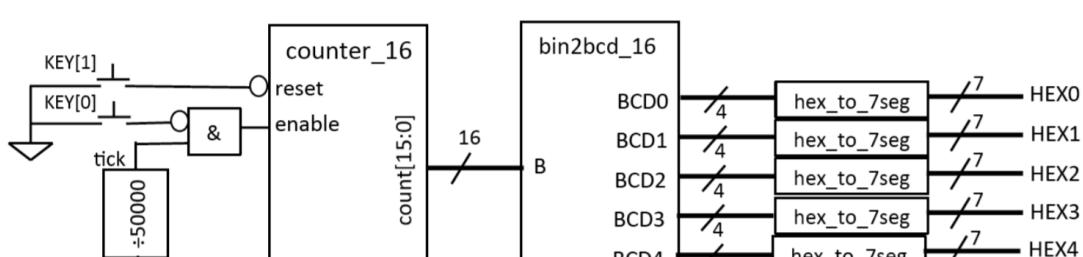



To extend this to a cascade counter, the next step was to design a tick module to allow the count to change every millisecond. The way this module works is to output high (**tick = 1'b1**) every 50,000 clock cycles as the enable signal into our 16-bit counter. Below is the code for out clock tick

```
module clk_16_tick( //DIVIDE BY 50 000
    clkin,
    tick);
parameter N_BIT = 16;
input clkin;
output tick;
reg [N_BIT-1:0] count;
reg tick;

initial tick = 1'b0;
initial count = 0;

always @ (posedge clkin)
begin
    if (count == 16'b1100001101010000) // 16'b1100001101010000 = 50,0000 IN DECIMAL
        begin
            tick <= 1'b1;
            count <= 0;
        end
    else
        begin
            count <= count + 1'b1;
            tick <= 1'b0;
        end
    end
endmodule
```

After creating the `clk_16_tick` module, the next step was to wire together the modules in the top-level specification.

```
module ex6_top(
    CLOCK_50,
    KEY,
    HEX0,HEX1,HEX2,HEX3,HEX4,
);
    input CLOCK_50;
    input [1:0] KEY;
    output [6:0] HEX0;
    output [6:0] HEX1;
    output [6:0] HEX2;
    output [6:0] HEX3;
    output [6:0] HEX4;

    //Top level module only has KEY,CLOCK and HEX as in/outputs

    //output [3:0] BCD0;
    //output [3:0] BCD1;
    //output [3:0] BCD2;
    //output [3:0] BCD3;
    //output [3:0] BCD4;
    //output [15:0] count;

    //input and outputs are only for the inputs into the module and outputs
    //wires are used to connect input and output ports of a module instantiation

    wire [3:0] BCD0;
    wire [3:0] BCD1;
```

```

    wire [3:0] BCD2;
    wire [3:0] BCD3;
    wire [3:0] BCD4;
    wire [15:0] count;
    wire tick, enable;

clk_16_tick      TICK (CLOCK_50, tick); //count up to 50000
assign enable = (tick & ~KEY[0]); //Key[0] is active low

counter_16      CNTR (CLOCK_50,enable,~KEY[1],count);
bin2bcd_16      CVRT (count,BCD0,BCD1,BCD2,BCD3,BCD4);
hex_to_7seg     SEGO (HEX0, BCD0);
hex_to_7seg     SEG1 (HEX1, BCD1);
hex_to_7seg     SEG2 (HEX2, BCD2);
hex_to_7seg     SEG3 (HEX3, BCD3);
hex_to_7seg     SEG4 (HEX4, BCD4);

endmodule

```


We had the problem of instantiating individual module inputs/outputs as **input/output** instead of wires but after understanding the purpose of **wire**, the implementation of the top-module in Verilog became simple. We also had pay attention to the fact **KEY** is active low so we needed to negate (\sim) it when assigning enable.

Experiment 7: Linear Feedback Shift Register (LFSR) and PRBS

Sunday, December 8, 2019 1:52 PM

In Experiment 7, we were required to design a 7 bit LFSR implementing the polynomial $1 + X + X^7$, initializing the shift register to 7'b1 to generate a pseudo random binary sequence (PRBS).

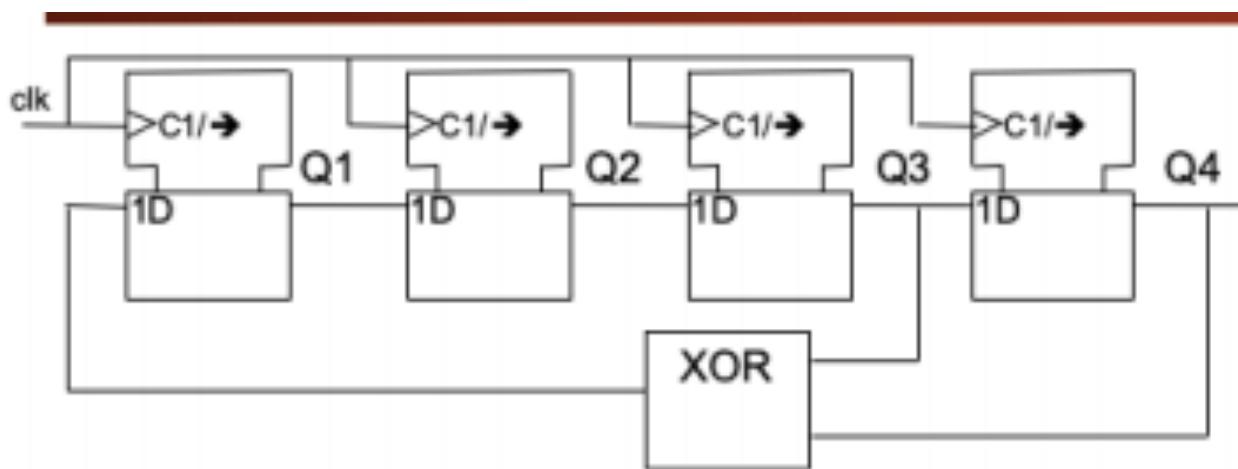We first recall the polynomial we came across in Lecture 5, for $1 + X^3 + X^4$



It is important to note that the shift register must be initialized to 1 as beginning at 0 causes the count to remain stuck at 0. In our current case, this will constantly shift 0s into the LSB and never change the value of SREG[1] ^ SREG[7].

We understood that to implement the polynomial, we had to XOR the bits we required together.

The first step was to build a module to perform the LFSR:

```
module lfsr_7(
    enable,
    clock,
    out
);
    input clock;
    input enable;
    output [7:1] out;
    reg[7:1] sreg;
```

```

initial sreg = 7'b1;
always @ (posedge clock)
begin
  if (enable==1'b1)
    sreg<= {sreg[6:1], sreg[7] ^ sreg[1]};
  end
assign out = sreg;
endmodule

```

Afterwards the only thing that was left was to wire up the top-level design specification.

```

module ex7_top(
  CLOCK_50,
  HEX0,      //Hex output on segment display
  HEX1,
  KEY
);
  input CLOCK_50;
  input [3:3]KEY;
  output [6:0]HEX0;
  output [6:0]HEX1;

  wire [6:0] sreg_out;
  wire enable;

  assign enable = ~KEY[3]; //Key[3] is active low

  lfsr_7 shift(enable, CLOCK_50, sreg_out);

  hex_to_7seg    SEG0(HEX0,sreg_out[3:0]);
  hex_to_7seg    SEG1(HEX1,sreg_out[6:4]);

endmodule


```

It is also important to note that although the shift register is defined as having 7 output bits, it actually has 8 bits with the 0th bit being simulated by the SREG[1] ^ SREG[7] output. Hence why the bits of the bits of the output **out** (which has been assigned to SREG) must be refined as [7:1] instead of [6:0].

Experiment 8 (Optional): Starting line delay circuit

Sunday, December 8, 2019 1:53 PM

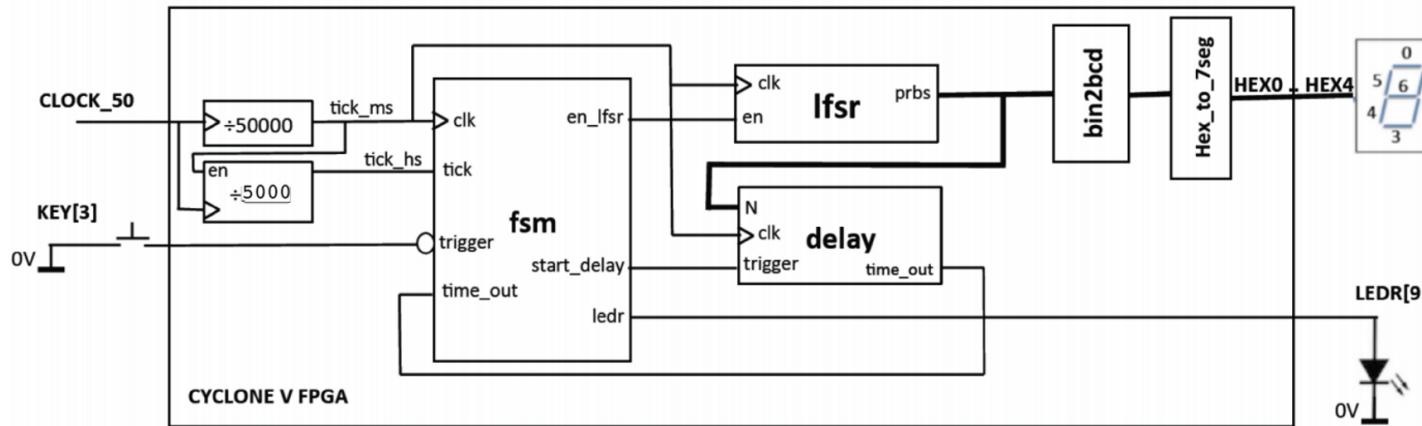For the optional Experiment 8, we were tasked with designing a starting line delay circuit. To do this, we will use the following components:



- The circuit is triggered by pressing KEY[3]
 - The 10 LEDs will then light up from left to right at 0.5 second intervals until all the LEDs turn off
 - The circuit then waits for a random period (as specified by the LFSR) for between 0.25 and 1 second before the next sequence begins
 - Then the display will show the random delay period in milliseconds on five 7 segment displays

Design decisions

Before embarking on the Experiment, several design decisions needed to be made:

1. How many bits LFSR is required?

We decided on 6 bits, for two reasons:

- a. We needed to start at 0.25 seconds, and end at 16. If we step each time by 0.25, $16/0.25 = 64$ different values, which is the size of 6 bits.
 - b. This also allowed us to make use of code modularity, by taking our previous work.

2. How many bits should we use in the delay module?

The range of timing delay is from 0.25 to 16,000 milliseconds. Hence we need 14 bits which of 16,384ms ~ 16,000ms

The important modules for this experiment which have not been introduced to us yet through Delay modules:

TOP FUNCTION

The schematic is shown

/1
2

:0]

Os are ON

5 and 16 seconds before all

displays

, we would therefore need

rk on the polynomial 1

allows us to get a maximum

gh the Labs are the FSM and

The important modules for this experiment which have not been introduced to us yet through the Labs are the FSM and Delay modules:

TOP FUNCTION

```
1  module ex8_top(
2    CLOCK_50,
3    KEY,
4    HEX0,
5    HEX1,
6    HEX2,
7    HEX3,
8    HEX4,
9    LEDR);
10
11   input CLOCK_50;
12   input [3:0] KEY;
13
14   output [6:0] HEX0, HEX1, HEX2, HEX3, HEX4;
15
16   wire TICK_1MS, TICK_500MS;
17   wire time_out;
18   wire en_lfsr, start_delay;
19   wire [6:0] prbs;
20   wire [3:0] BCD0, BCD1, BCD2, BCD3, BCD4;
21
22   clk_16_tick TICK1(CLOCK_50, TICK_1MS);
23   clk500 TICK500(TICK_1MS,TICK_500MS);
24   lfsr_7 RDMGEN(en_lfsr, TICK_1MS, prbs);
25
26   fsm_light FSM(TICK_1MS, TICK_500MS, ~KEY[3], time_out, en_lfsr, start_delay, LEDR[9:0]);
27
28   //Random delay generation
29   delay DELAY(TICK_1MS, start_delay,(prbs*125),time_out);
30
31   //Number conversions for 7 seg display
32   bin2bcd_16((prbs*125),BCD0, BCD1, BCD2, BCD3, BCD4);
33   hex_to_7seg SEG0(HEX0,BCD0);
34   hex_to_7seg SEG1(HEX1,BCD1);
35   hex_to_7seg SEG2(HEX2,BCD2);
36   hex_to_7seg SEG3(HEX3,BCD3);
37   hex_to_7seg SEG4(HEX4,BCD4);
38
39 endmodule
40
41
42
```

LFSR

```
module lfsr_7(
  enable,
  clock,
  out
);

  input clock;
  input enable;
  output [7:1] out;

  reg[7:1] sreg;
  initial sreg = 7'b1;
  always @ (posedge clock)
    begin
```

```

    if'(enable==1'b1)
        sreg<= {sreg[6:1], sreg[7] ^ sreg[1]};
    end
    assign out = sreg;
endmodule

```

Delay

```

module delay(
sysclk,
trigger,
n,
time_out);

//Define number of bits in delay counter
parameter BIT_SZ = 16;

//Ports
input sysclk, trigger;
input [BIT_SZ-1:0] n;
output time_out;

//reg declaration
reg[BIT_SZ-1:0] count;
reg time_out;

always @ (posedge sysclk)
begin
    if(trigger==1'b1)
    begin
        if(count==n)
            time_out <= 1'b1;
        else
            count <= count + 1'b1;
    end
    else
    begin
        count <= 0;
        time_out <= 0;
    end
end

```

endmodule //end of module

FSM

Designing the FSM proved to be the most difficult section of this task because it involves many different steps

```
input clk, tick, trigger, time_out;
```

```

output en_lfsr, start_delay;
output [9:0] ledr;

reg [9:0] ledr;
reg en_lfsr, start_delay;

//Defining each of our states using one-hot encoding
parameter IDLE = 11'b000000000001;
parameter LIGHT0 = 11'b000000000010;
parameter LIGHT1 = 11'b0000000000100;
parameter LIGHT2 = 11'b0000000001000;
parameter LIGHT3 = 11'b0000000010000;
parameter LIGHT4 = 11'b000000100000;
parameter LIGHT5 = 11'b0000010000000;
parameter LIGHT6 = 11'b0001000000000;
parameter LIGHT7 = 11'b0010000000000;
parameter LIGHT8 = 11'b0100000000000;
parameter LIGHT9 = 11'b1000000000000;

//setting up initial state for switch case
reg [10:0] state;
initial state = IDLE;
initial en_lfsr = 1'b0;
initial start_delay = 1'b0;

//transitions
always @ (posedge tick)
begin
    case(state)
        IDLE: if(trigger == 1'b1) state<= LIGHT0;
        LIGHT0: if(tick == 1'b1) state <= LIGHT1;
        LIGHT1: if(tick == 1'b1) state <= LIGHT2;
        LIGHT2: if(tick == 1'b1) state <= LIGHT3;
        LIGHT3: if(tick == 1'b1) state <= LIGHT4;
        LIGHT4: if(tick == 1'b1) state <= LIGHT5;
        LIGHT5: if(tick == 1'b1) state <= LIGHT6;
        LIGHT6: if(tick == 1'b1) state <= LIGHT7;
        LIGHT7: if(tick == 1'b1) state <= LIGHT8;
        LIGHT8: if(tick == 1'b1) state <= LIGHT9;
        LIGHT9: if(time_out == 1'b1) state <= IDLE;
        default: ;
    endcase
end

//output for each state
always @ (*)
begin
    case(state)
        IDLE: begin //no lights
            ledr <= 10'b0000000000;
            en_lfsr <= 1'b1; //request random number
            start_delay <= 1'b0;
        end
        LIGHT0: begin //start lights
            ledr <= 10'b1000000000; //LED9
            en_lfsr <= 1'b0;
            start_delay <= 1'b0;
        end
        LIGHT1: begin
            ledr <= 10'b1100000000; //LED9-8
            en_lfsr <= 1'b0;
            start_delay <= 1'b0;
        end
    endcase
end

```

```

        endu
LIGHT2: begin
    ledr <= 10'b1110000000; //LED9-7
    en_lfsr <= 1'b0;
    start_delay <= 1'b0;
end
LIGHT3: begin
    ledr <= 10'b1111000000; //LED9-6
    en_lfsr <= 1'b0;
    start_delay <= 1'b0;
end
LIGHT4: begin
    ledr <= 10'b1111100000; //LED9-5
    en_lfsr <= 1'b0;
    start_delay <= 1'b0;
end
LIGHT5: begin
    ledr <= 10'b1111110000; //LED9-4
    en_lfsr <= 1'b0;
    start_delay <= 1'b0;
end
LIGHT6: begin
    ledr <= 10'b1111111000; //LED9-3
    en_lfsr <= 1'b0;
    start_delay <= 1'b0;
end
LIGHT7: begin
    ledr <= 10'b1111111100; //LED9-2
    en_lfsr <= 1'b0;
    start_delay <= 1'b0;
end
LIGHT8: begin
    ledr <= 10'b1111111110; //LED9-1
    en_lfsr <= 1'b0;
    start_delay <= 1'b0;
end
LIGHT9: begin
    ledr <= 10'b1111111111; //LED9-0
    en_lfsr <= 1'b0;
    start_delay <= 1'b1;
end

default: ;
endcase
end
endmodule

```




Experiment 9 (Optional): A reaction meter

Sunday, December 8, 2019 1:53 PM

For Experiment 9, we were tasked with incorporating a Reaction Meter into our design from scratch. The reaction meter should count the time between all the LEDs turning OFF and the user pressing KEY[0]. The reaction time, including a random delay, is then output on the 7 segment displays.

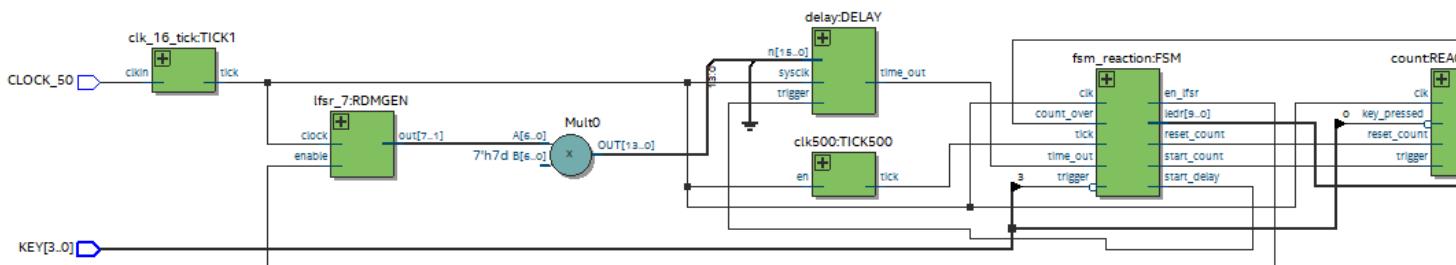
After analyzing the task, we decided that a **count** module to measure the reaction time of the reaction meter was required. The schematic of our final design can be seen below:



This meant that we required extra outputs from the FSM to control the enable and reset of the count module, as well as an additional trigger signal for KEY[0]. The first step was to design the count module:

COUNT
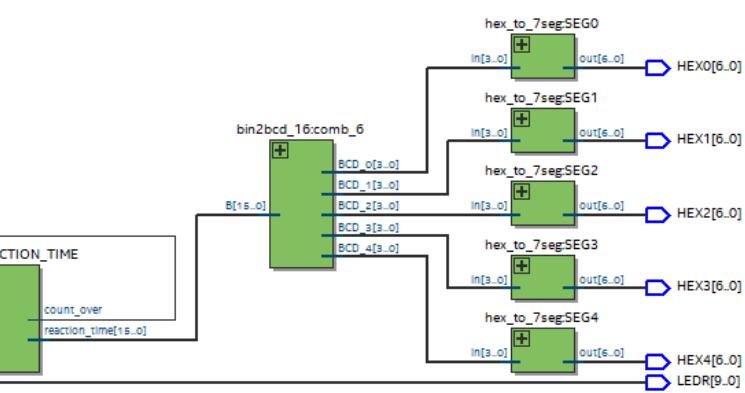
```
module count(clk, key_pressed, trigger, reset_count, reaction_time, count_over);  
  input clk; // input clk is tick_1ms  
  input key_pressed; // input [3:0] KEY;  
  input trigger;  
  input reset_count;  
  output count_over;
```



```

      input reset_count;
      output count_over;

parameter BIT_SZ = 16;
output reg [BIT_SZ-1:0] reaction_time;

initial reaction_time = 0;
reg count_over;

always @ (posedge clk)
  if (reset_count == 1'b1) // key not pressed
    reaction_time <= 0;
  else if (trigger == 1'b1 && key_pressed == 0) // key not pressed
begin
  reaction_time <= reaction_time + 1'b1;
  count_over <= 0;
end
else if (trigger == 1'b1 && key_pressed == 1'b1) // key pressed
count_over <= 1;

endmodule

```

The next step was to edit the FSM to incorporate the addition of the count module.

FSM

```

input clk, tick, trigger,time_out;
output en_lfsr, start_delay;
output [9:0] ledr;

input count_over;
output reg start_count;
output reg reset_count;

reg [9:0] ledr;
reg en_lfsr, start_delay;

//Defining each of our states using one-hot encoding
parameter IDLE = 12'b00000000000001;
parameter LIGHT0 = 12'b00000000000010;
parameter LIGHT1 = 12'b00000000000100;
parameter LIGHT2 = 12'b00000000001000;
parameter LIGHT3 = 12'b00000000010000;
parameter LIGHT4 = 12'b00000000100000;
parameter LIGHT5 = 12'b00000001000000;
parameter LIGHT6 = 12'b00000100000000;
parameter LIGHT7 = 12'b00010000000000;
parameter LIGHT8 = 12'b00100000000000;
parameter LIGHT9 = 12'b01000000000000;
parameter REACTION = 12'b10000000000000;

//setting up initial state for switch case
reg [11:0] state;
initial state = IDLE;
initial en_lfsr = 1'b0;

```

```

initial start_delay = 1'b0;
initial start_count = 1'b0;
initial reset_count = 1'b0;

//transitions
always @ (posedge tick)
begin
    case(state)
        IDLE: if(trigger == 1'b1) state<= LIGHT0;
        LIGHT0: if(tick == 1'b1) state <= LIGHT1;
        LIGHT1: if(tick == 1'b1) state <= LIGHT2;
        LIGHT2: if(tick == 1'b1) state <= LIGHT3;
        LIGHT3: if(tick == 1'b1) state <= LIGHT4;
        LIGHT4: if(tick == 1'b1) state <= LIGHT5;
        LIGHT5: if(tick == 1'b1) state <= LIGHT6;
        LIGHT6: if(tick == 1'b1) state <= LIGHT7;
        LIGHT7: if(tick == 1'b1) state <= LIGHT8;
        LIGHT8: if(tick == 1'b1) state <= LIGHT9;
        LIGHT9: if(time_out == 1'b1) state <= REACTION;
        REACTION: if(count_over == 1'b1) state <= IDLE;
        default: ;
    endcase
end

//output for each state
always @ (*)
begin
    case(state)
        IDLE: begin //no lights
            ledr <= 10'b0000000000;
            en_lfsr <= 1'b1; //request random number
            start_delay <= 1'b0;
            start_count <= 1'b0;
            reset_count <= 1'b0;
        end
        LIGHT0: begin //start lights
            ledr <= 10'b1000000000; //LED9
            en_lfsr <= 1'b0;
            start_delay <= 1'b0;
            start_count <= 1'b0;
            reset_count <= 1'b1;
        end
        LIGHT1: begin
            ledr <= 10'b1100000000; //LED9-8
            en_lfsr <= 1'b0;
            start_delay <= 1'b0;
            start_count <= 1'b0;
            reset_count <= 1'b0;
        end
        LIGHT2: begin
            ledr <= 10'b1110000000; //LED9-7
            en_lfsr <= 1'b0;
            start_delay <= 1'b0;
            start_count <= 1'b0;
            reset_count <= 1'b0;
        end
        LIGHT3: begin
            ledr <= 10'b1111000000; //LED9-6
            en_lfsr <= 1'b0;
            start_delay <= 1'b0;
            start_count <= 1'b0;
            reset_count <= 1'b0;
        end
        LIGHT4: begin
            ledr <= 10'b1111100000; //LED9-5
            en_lfsr <= 1'b0;
            start_delay <= 1'b0;
            start_count <= 1'b0;
            reset_count <= 1'b0;
        end
    endcase
end

```


```


      end
LIGHT5: begin
    ledr <= 10'b1111110000; //LED9-4
    en_lfsr <= 1'b0;
    start_delay <= 1'b0;
    start_count <= 1'b0;
    reset_count <= 1'b0;
end
LIGHT6: begin
    ledr <= 10'b1111111000; //LED9-3
    en_lfsr <= 1'b0;
    start_delay <= 1'b0;
    start_count <= 1'b0;
    reset_count <= 1'b0;
end
LIGHT7: begin
    ledr <= 10'b1111111100; //LED9-2
    en_lfsr <= 1'b0;
    start_delay <= 1'b0;
    start_count <= 1'b0;
    reset_count <= 1'b0;
end
LIGHT8: begin
    ledr <= 10'b1111111110; //LED9-1
    en_lfsr <= 1'b0;
    start_delay <= 1'b0;
    start_count <= 1'b0;
    reset_count <= 1'b0;
end
LIGHT9: begin
    ledr <= 10'b1111111111; //LED9-0
    en_lfsr <= 1'b0;
    start_delay <= 1'b1;
    start_count <= 1'b0;
    reset_count <= 1'b0;
end
REACTION: begin
    ledr <= 10'b0000000000; //LED OFF
    en_lfsr <= 1'b0;
    start_delay <= 1'b0;
    start_count <= 1'b1;
    reset_count <= 1'b0;
end
default: ;
endcase
end


endmodule

```

This provided us with the following state diagram:

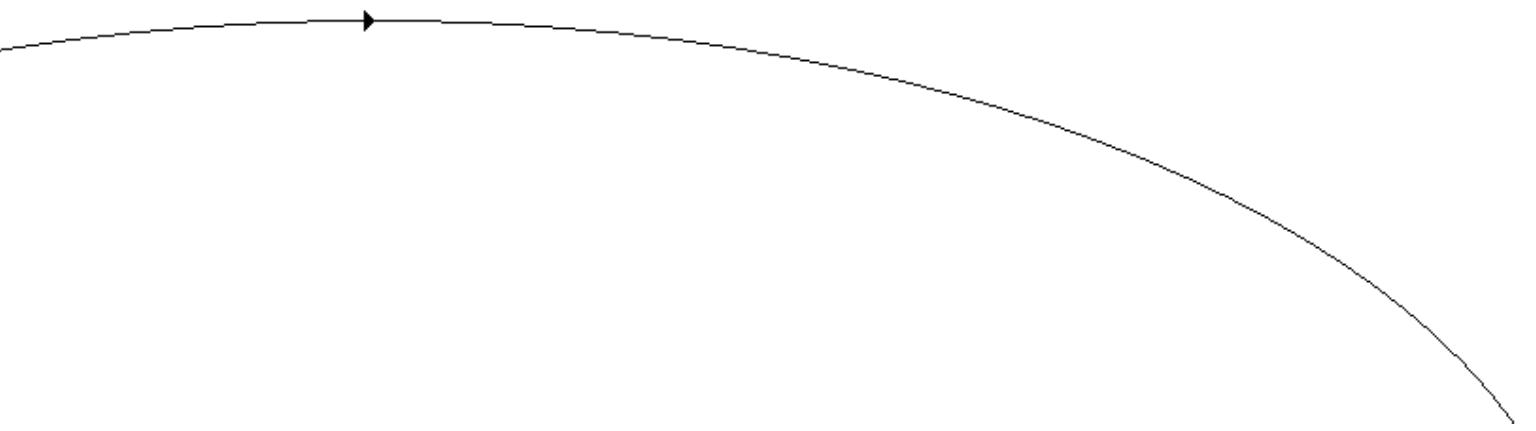

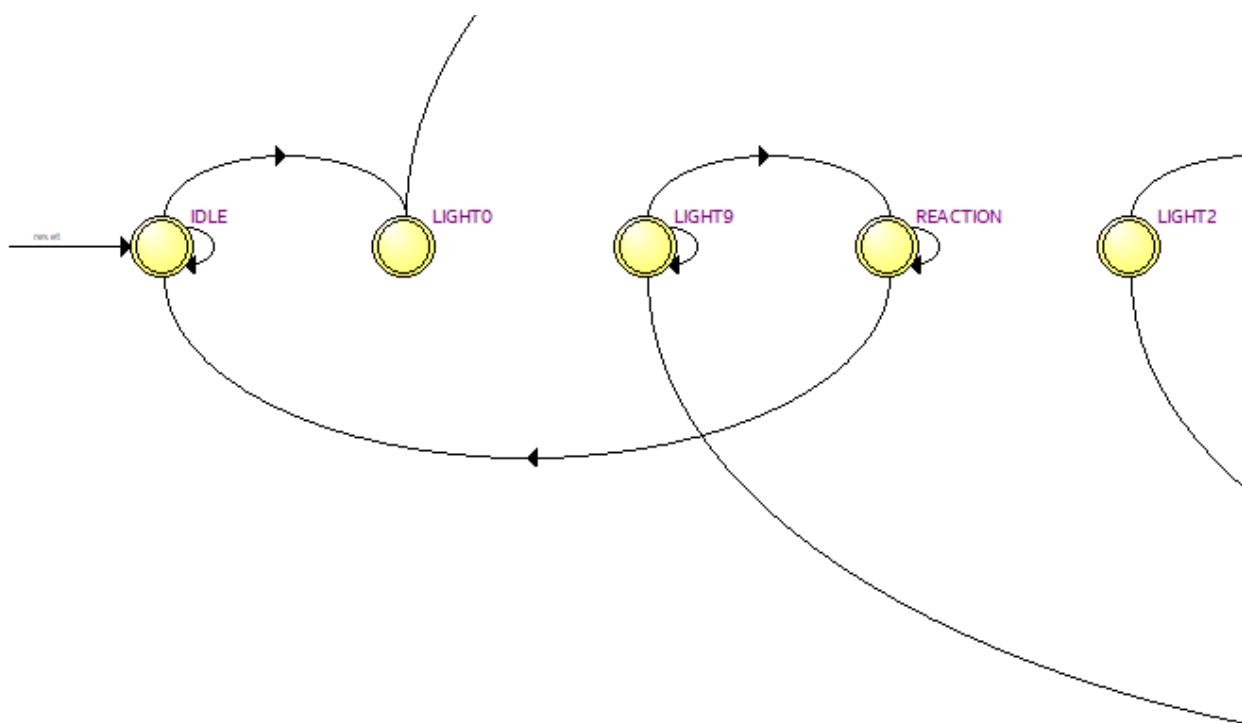

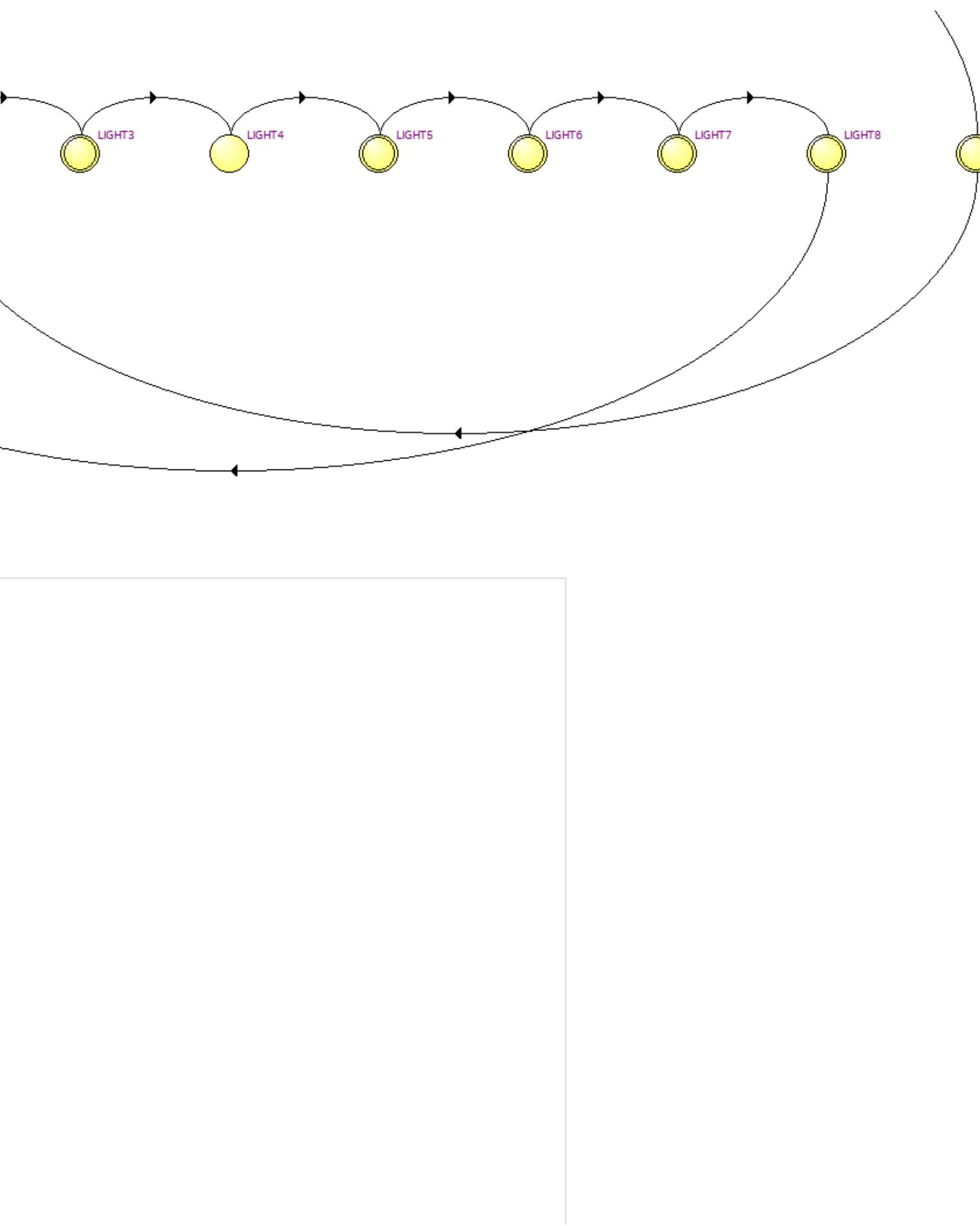

LIGHT1

Experiment 10: Interface with the MCP4911 Digital Converter

Sunday, December 8, 2019 1:53 PM

We began this experiment looking at the add-on card to the DE1 board. It held a 10-bit ADC sockets for each.

Having our own add-on card unique to the course was extremely beneficial, as it gave us an interface with the peripherals of our FPGA using the SPI.

The focus of this experiment was thus to introduce us to:

- Understanding and verifying the **operation of the Serial-to-Parallel Interface (SPI)** of the converter (DAC) MCP4911 using Modelsim
- Testing the DAC and **measured its output voltage range**

The focus was on understanding our MCP4911 Digital-to-Analogue Converter. As with all for understand it's behavior before proceeding. For that reason, we started by looking at our da

MCP4901/4911/4921

1.0 ELECTRICAL CHARACTERISTICS

Absolute Maximum Ratings †

V _{DD}	6.5V
All inputs and outputs w.r.t	V _{SS} -0.3V to V _{DD} +0.3V
Current at Input Pins	±2 mA
Current at Supply Pins	±50 mA
Current at Output Pins	±25 mA
Storage temperature	-65°C to +150°C
Ambient temp. with power applied	-55°C to +125°C
ESD protection on all pins	≥ 4 kV (HBM), ≥ 400V (MM)
Maximum Junction Temperature (T _J)	+150°C

† **Notice:** Stresses above those listed under "Maximum Ratings" may cause permanent damage to the device. This is a stress rating only and functional operation of the device at those or any other conditions above those indicated in the operational listings of this specification is not implied. Exposure to maximum rating conditions for extended periods may affect device reliability.

ELECTRICAL CHARACTERISTICS

Electrical Specifications: Unless otherwise indicated, V_{DD} = 5V, V_{SS} = 0V, V_{REF} = 2.048V, Output Buffer Gain (G) = 2x, R_L = 5 kΩ to GND, C_L = 100 pF T_A = -40 to +85°C. Typical values are at +25°C.

Parameters	Sym	Min	Typ	Max	Units	Conditions
Power Requirements						
Operating Voltage	V _{DD}	2.7	—	5.5	—	
Supply Current	I _{DD}	—	175	350	µA	V _{DD} = 5V

-to-Analogue

and 10-bit DAC, along with

insight into how we can

the digital-to-analogue


foreign devices, we should first
datasheet.

		—	125	250	μA	$V_{DD} = 5\text{V}$ V_{REF} input is unbuffered, all digital inputs are grounded, all analog outputs (V_{OUT}) are unloaded. Code = 0x000h
--	--	---	-----	-----	---------------	---

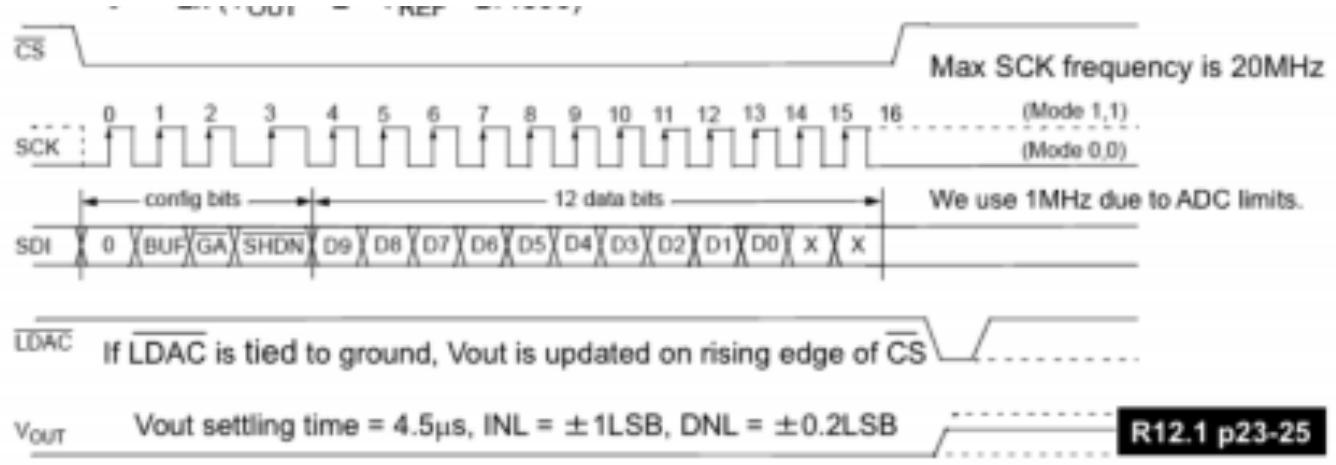1. Understanding datasheet

We were able to synthesize the datasheet information as follows:

- PURPOSE OF DAC PINS
 - V_{DD} , power on.
 - V_{SS} , power reset
 - Chip Select (CS) signal goes low, indicating start of data
 - SDI, serial data input, the stream of 15 bits that are sampled
 - By the clock, SCK
- Information sent to the DAC using SDI pin:



- DAC configuration: first bit set to zero, config bits until clock 3.
 - Remaining 12 bits used for data, which is to be converted to analog information
 - BUF: set to 1 for transfer of voltage
 - GA set to 0 as Electrical specification states it is Output Buffer Gain of 2x
 - Bit 12: SHDN, set to 1 as we are using the DAC.

2. Timing Diagram

Having understood the general functions of our datasheet, we were now concerned with our module and its interaction with said DAC.

Understanding that the spi2dac module takes a 10-bit number in parallel, and generates serial data, we drew a timing diagram to assert our understanding of this for the word 10'h23b.


We proceed to developing the timing diagram, in the hopes of understanding the flow of our

our Verilog module spi2dac

serial signals to drive the DAC,

our module.

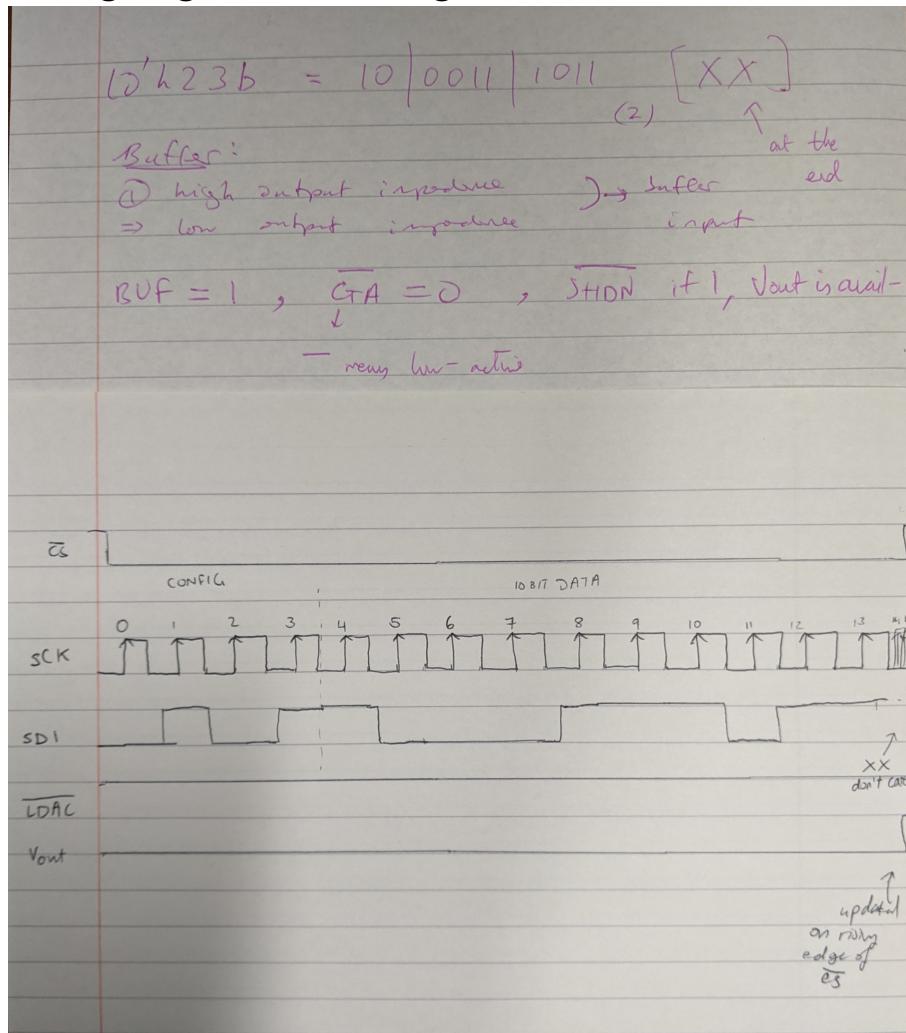Timing diagram for sending of 10'h23b word





We felt we had some sort of intuition, but now really wanted to see that we were getting a

3. Timing diagram on Modelsim

To first generate a timing diagram, we had to set the parameters for our testbench. This was generated our clock and other signal values as follows.

INSERT DO FILE

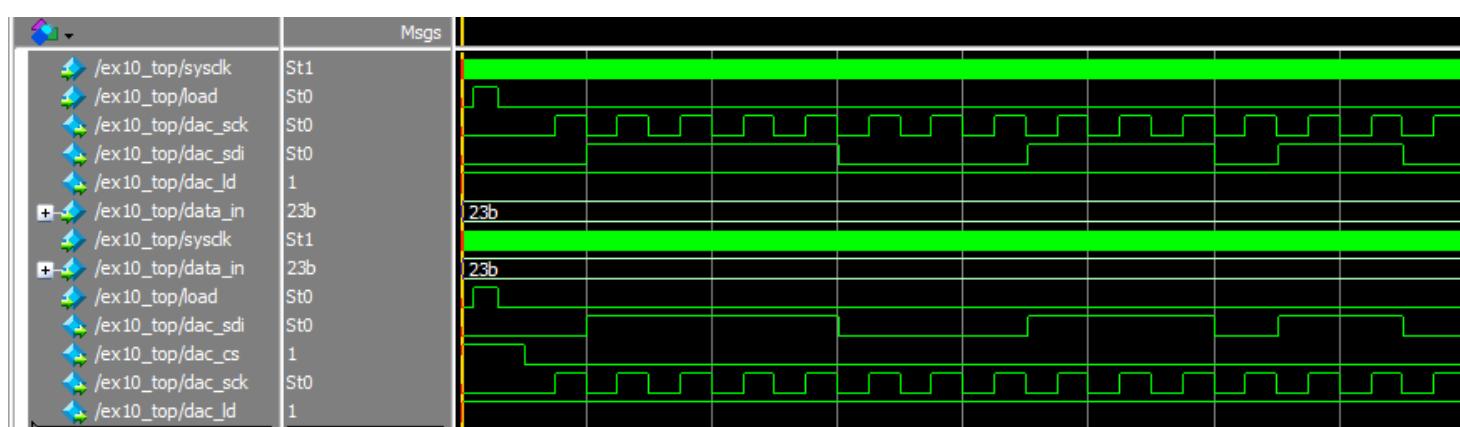

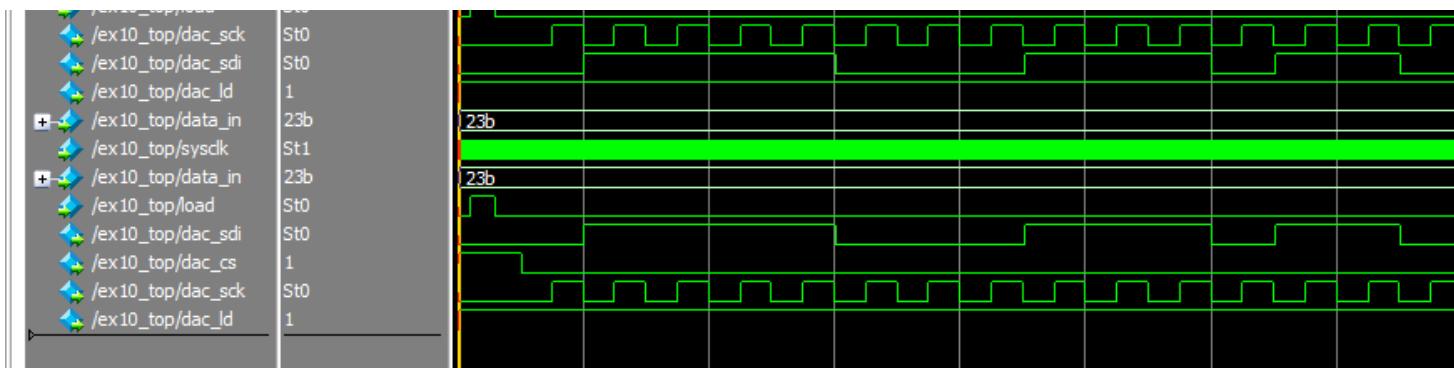

Our timing diagram was correct for the most part, bar our 3rd config bit- ~GA. We thought to follow what was said in the datasheet: "2x unless otherwise stated". However we understood that in fact ~GA meant it should be set to 0 if we want to shutdown our device to conserve power, and should be one if we are using the DAC.


From the datasheet, we believed that this bit should be 1 for MCP4911. It was only after seeing it in reality with our spi2dac module did we understand that in our timing diagram it should have been 1. This displayed a real strength of Modelsim to visualize the behavior of our program.


After understanding our data signals and viewing their correct waveforms, we needed to test our DAC on DE1.

4. Testing DAC on DE1

After completing our pin assignment and assigning our given top-level entity, we proceeded to place & route our design.

Successful Place & Route

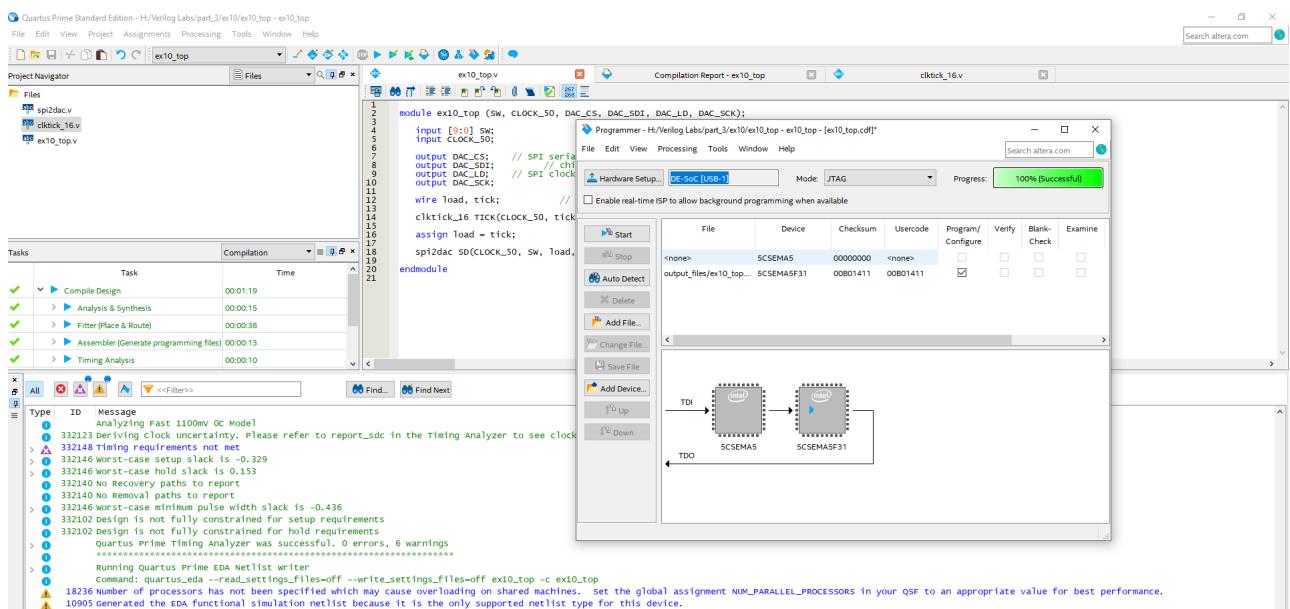

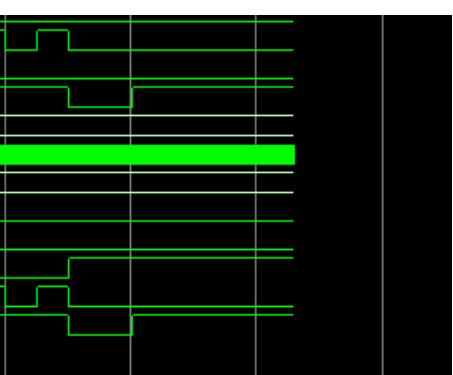

```
204019 Generated file ex10_top.vo in folder "H:/Verilog Labs/part_3/ex10/simulation/modelsim/" for EDA simulation tool  
> Quartus Prime EDA Netlist writer was successful. 0 errors, 2 warnings  
293000 Quartus Prime FULL compilation was successful. 0 errors, 81 warnings
```

System (21) Processing (127)


100% 00:01:19

Everything worked fine... on the surface! It would take an analysis of our analogue out signal to truly know whether it was working or not.

5. Verifying signals on oscilloscope

After triggering our signal on our scope, we were very happy to see our word 10'h23b was sent to our DAC! It was shown here on our DAC output.

DAC OUTPUT FOR SW SET TO 23B

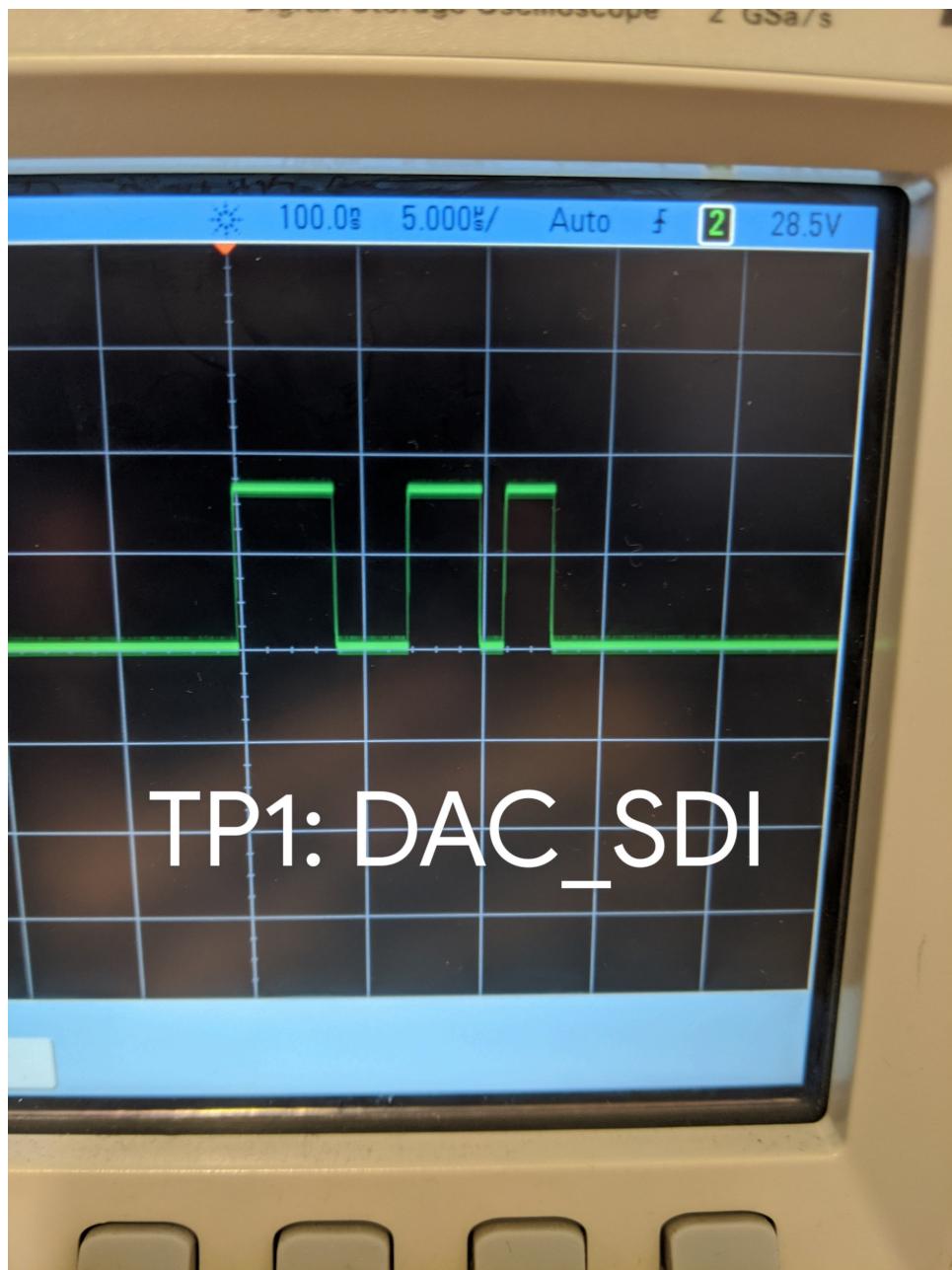

Experiment 11: D-to-A conversion u

Sunday, December 8, 2019 1:54 PM


Key outcome from this experiment:

- Test the DAC and **measure its output voltage range**

An alternative to using a DAC chip (SPI serial interface to communicate with chip), we could generate analogue output from a digital number using pulse-width modulation (PWM).

Whilst the concept of a varying width displaying a real signal seemed difficult at first, the implementation is in fact quite straightforward, making it a clearly useful tool if we had no resources to set up a dedicated DAC chip.

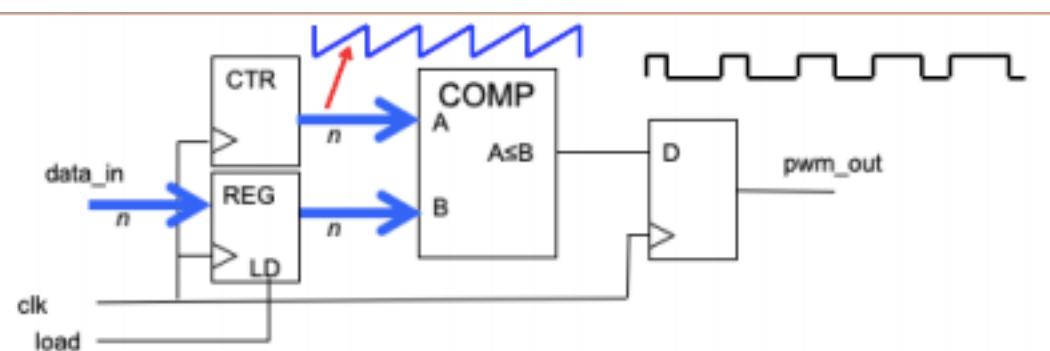The block diagram of a PWM is as follows:



And the Verilog code is even more simple:

```
module pwm(CLOCK_50, SW, Load, pwm_out);  
  input CLOCK_50; //system clock  
  input [9:0] SW; //input data for conversion  
  input Load; //high pulse to load  
  output pwm_out; //PWM output  
  
  reg [9:0] d; //internal register  
  reg [9:0] count; //internal 10-bit counter  
  reg pwm_out;  
  
  always @ (posedge CLOCK_50)  
    if (Load == 1'b1) d <= SW;
```

sing pulse modulation

I'd just directly produce an

implementation in Verilog was
to set up the SPI interface with the

```

initial count = 10'b0;

always @ (posedge CLOCK_50) begin
    count <= count + 1'b1;
    if(count > d)
        pwm_out <= 1'b0;
    else
        pwm_out <= 1'b1;
end
endmodule

```

We had two questions

1. What was the effect of the low-pass filter in this circuit?
2. How would the voltage range change from the DAC vs. PWM?


Examine signals at TP5 & TP8

- TP5 – gives us our pw5_out before the low pass filter
- TP5 - analogue out right channel (after passing though the add-on board)

Compare output voltage ranges at TP8 & TP9:

- TP8 ranges from -0.17V to 3.10V
- TP9 ranges from 40mv to 3.38V (TP5 ranges from 3.30V to 3.47V)

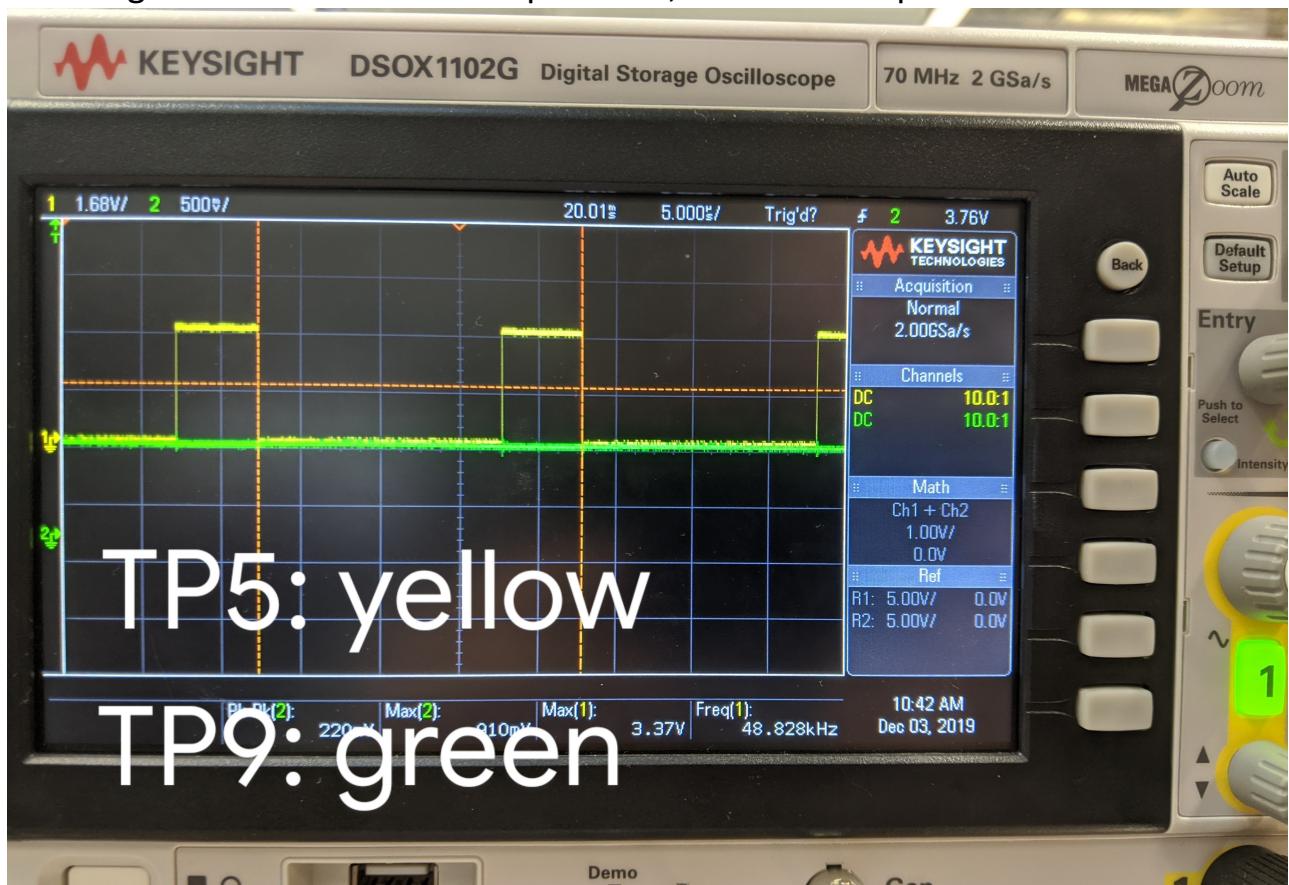
We sought out to answer these questions, and first compared TP5 to TP9 to see the effect






We looked into TP5 further to understand how PWM affects the pulse width.

The higher the bit, the wider the pulse.

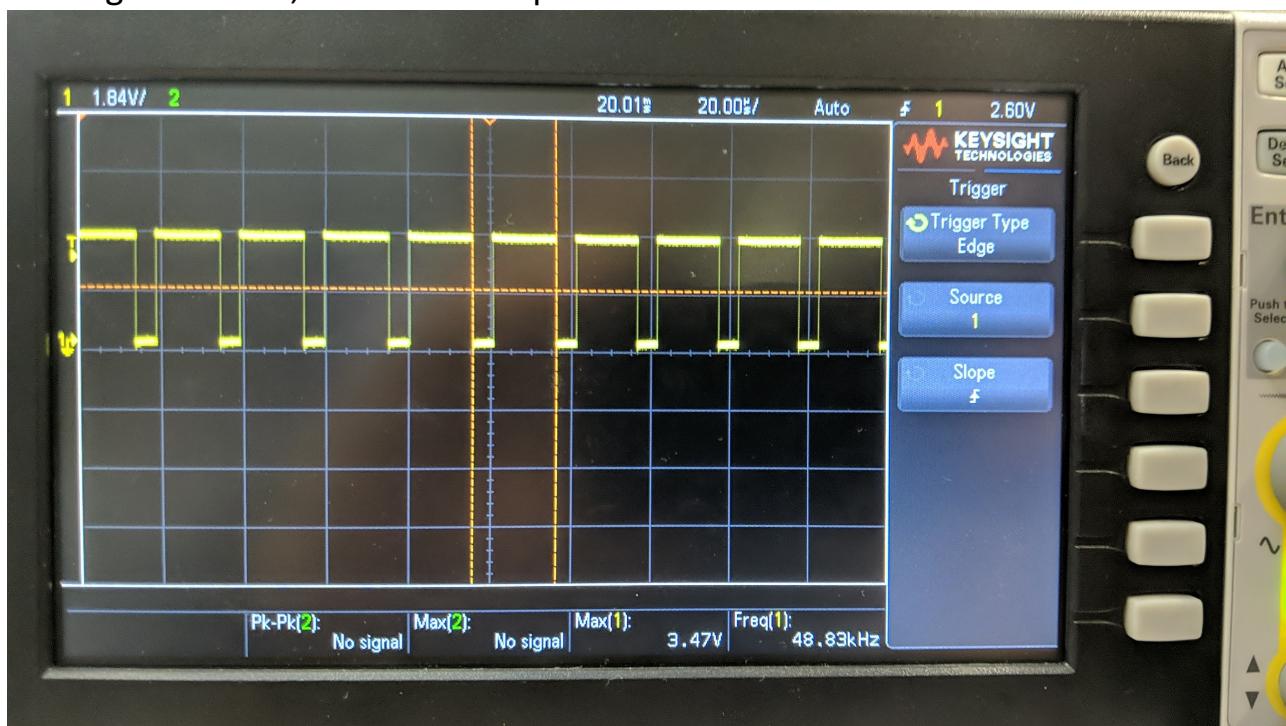

This leads to a higher value at TP8

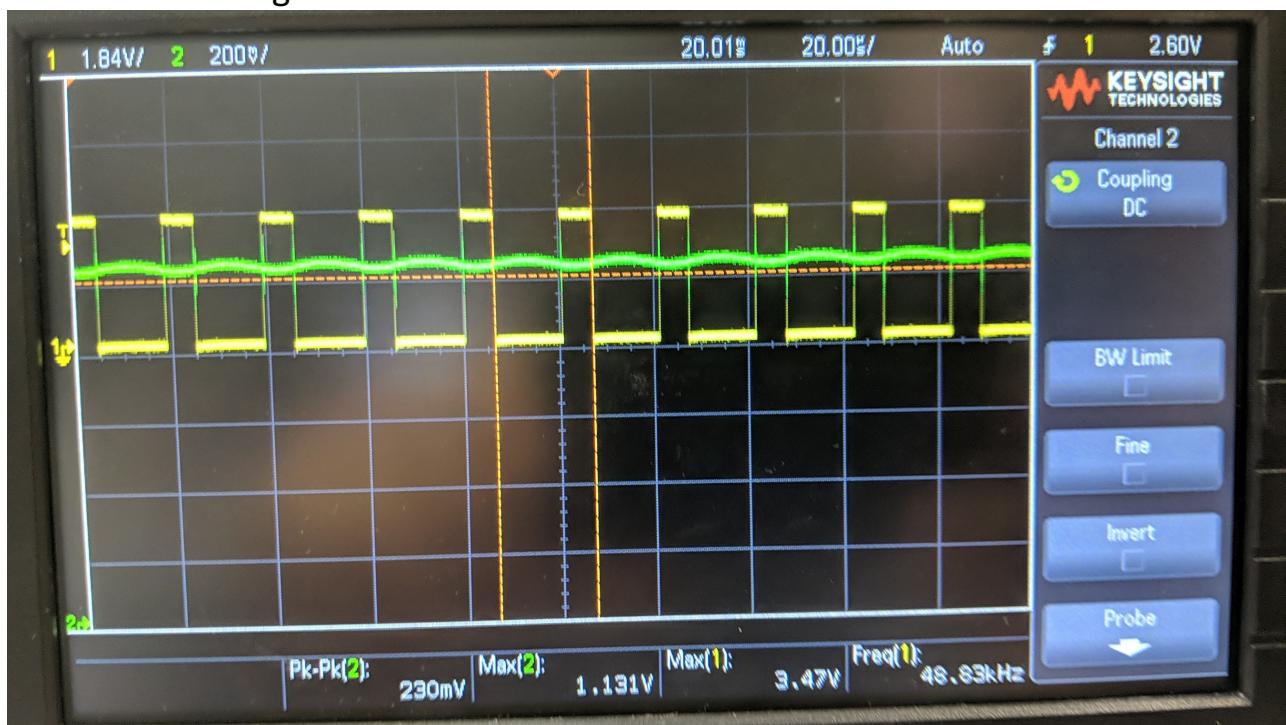

Displaying to us the effect of PWM on DAC.

Experiment 12: Designing and testing a sinewave table in ROM

Sunday, December 8, 2019 1:55 PM

Key outcomes of Experiment 12:

- Work with using a **ROM** in Verilog

This experiment provides us with a new tool: the Read-Only Memory (ROM).

We will achieve our initial aim of learning how to use a **ROM** generating a table of sine values hard-coded into memory.

The relationship between the ROM content and address was given, as follows:

$$D[9:0] = \text{int}(511 * \sin(A[9:0] * 2 * \pi / 1024) + 512) \quad \text{for } 1023 \geq A[9:0] \geq 0$$

1. Understanding Memory Initialization

We are designing a 1K x 10 bit ROM (I.e. 1000 memory addresses, each holding 10bits). If we wanted to hard-code each value into this ROM ourselves, it could take a ~Veri~ long time! Besides the time factor, we are also much more prone to human errors if we hardcoded each address ourselves. Its clear some form of automation is necessary.

For that reason, our attention is drawn to the idea of Scripting. We were kindly provided with two scripts which essentially generate the same memory we are looking for:

Python Script

```
1 # sinegen.py - Generate sinewave table
2 # ... for use with Altera ROMs
3 #
4 from math import sin, cos, radians
5
6 DEPTH = 1024 # Size of ROM
7 WIDTH = 10   # Size of data in bits
8 OUTMAX = 2**WIDTH - 1 # Amplitude of sinewave
```

```

9
10 filename = "rom_data.mif"
11 f = open(filename,'w')
12
13 # Header for the .mif file
14 print >> f, "-- ROM Initialization file\n"
15 print >> f, "DEPTH = %d;" % DEPTH
16 print >> f, "WIDTH = %d;" % WIDTH
17 print >> f, "ADDRESS_RADIX = HEX;"
18 print >> f, "DATA_RADIX = HEX;\n"
19 print >> f, "CONTENT\nBEGIN\n"
20
21 ~ for address in range(DEPTH):
22     angle = (address*2*pi)/DEPTH
23     sine_value = sin(angle)
24     data = int((sine_value)*0.5*OUTMAX)+OUTMAX/2
25
26     print "%4x : %4x;" % (address, data)
27     print >> f, "%4x : %4x;" % (address, data)
28
29 print >> f, "END;\n"
30
31 f.close()
~
```

The function of this script is clear: it iteratively generates sine values and inputs them into our file "rom_data.mif"

Here's a general breakdown:

- Line 4 : necessary libraries for script operations
- Line 6-8: parameter values
- Line 14-19: .mif file header
- Line 21-2: calculation and inser
 - Calculation: for each address in ROM, calculate:

$$D[9:0] = \text{int}(511 * \sin(A[9:0] * 2 * \pi / 1024) + 512) \quad \text{for } 1023 \geq A[9:0] \geq 0$$

Having understood how the .mif file could be made automatically, we proceeded to look into whether the .mif file took

Addr	+0	+1	+2	+3	+4	+5	+6	+7
0c0	3D8	3D9	3DA	3DC	3DD	3DE	3DF	3E0

0c8	3E1	3E2	3E3	3E4	3E5	3E6	3E7	3E8
0d0	3E9	3EA	3EB	3EC	3EC	3ED	3EE	3EF
0d8	3F0	3F0	3F1	3F2	3F3	3F3	3F4	3F5
0e0	3F5	3F6	3F6	3F7	3F7	3F8	3F9	3F9
0e8	3F9	3FA	3FA	3FB	3FB	3FC	3FC	3FC
0f0	3FD	3FD	3FD	3FD	3FE	3FE	3FE	3FE
0f8	3FE	3FF						
100	3FF							
108	3FE	3FE	3FE	3FE	3FE	3FD	3FD	3FD
110	3FD	3FC	3FC	3FC	3FB	3FB	3FA	3FA
118	3F9	3F9	3F9	3F8	3F7	3F7	3F6	3F6
120	3F5	3F5	3F4	3F3	3F3	3F2	3F1	3F0
128	3F0	3EF	3EE	3ED	3EC	3EC	3EB	3EA
130	3E9	3E8	3E7	3E6	3E5	3E4	3E3	3E2

A quick glance at this data showed its periodic nature as the values tended upwards and downwards, suggesting a successful sinewave. Looking at numbers was nice, but as always- we can only be sure once we put it to test!

2. Practical testing of ROM functionality in Verilog

Having initialized our memory with the mif file, we were still interested in integrating it with our FPGA.

This started by creating our 1-port ROM in Verilog:

I/O sizes

```
module ROM (
    address,
    clock,
    q);
```

```

    input [9:0] address;
    input clock;
    output [9:0] q;
`ifndef ALTERA_RESERVED_QIS
// synopsys translate_off
endif
    tri1 clock;
`ifndef ALTERA_RESERVED_QIS
// synopsys translate_on
endif

    wire [9:0] sub_wire0;
    wire [9:0] q = sub_wire0[9:0];

```

1000 addresses (1024):

```
altsyncram_component.numwords_a = 1024,
```

Using our .mif file

```
altsyncram_component.init_file = "./rom_data.mif/rom_data.mif",
```

Having created our ROM 'block', we now had to integrate it into our program, where we could treat it as a regular module

```

1  module ex12_top(
2    CLOCK_50,
3    SW, HEX0, HEX1, HEX2, HEX3, HEX4
4  );
5    input CLOCK_50;
6    input [9:0] SW;
7    output [6:0] HEX0;
8    output [6:0] HEX1;
9    output [6:0] HEX2;
10   output [6:0] HEX3;
11   output [6:0] HEX4;
12
13   wire [9:0] ROM_OUT;
14   wire [3:0] BCD0, BCD1, BCD2, BCD3, BCD4;
15
16   ROM rom1(SW, CLOCK_50, ROM_OUT);
17
18   bin2bcd_16 display({6'b0,ROM_OUT},BCD0,BCD1, BCD2, BCD3, BCD4);
19
20   hex_to_7seg seg0(HEX0, BCD0);
21   hex_to_7seg seg1(HEX1,BCD1);
22   hex_to_7seg seg2(HEX2, BCD2);
23   hex_to_7seg seg3(HEX3, BCD3);
24   hex_to_7seg seg4(HEX4, BCD4);
25
26 endmodule

```

This top function is quite primitive. The steps can be summarized as follows:

1. Switches SW[9:0] correspond to Address A[9:0], which is used to access ROM
 - a. 50MHz clock allows us to access ROM value at clock edge (every 20ns)
2. Output of ROM, D[9:0], turned to BCD, then sent to 7-seg display

Experiment 13: A fixed frequency sinewave generator

Sunday, December 8, 2019 1:55 PM

Key outcomes of Experiment 13:


- Test the DAC and **measure its output voltage range**
- Work with using a **ROM** in Verilog

Instead of specifying and accessing a single ROM address, as in Exercise 12, what if we could access multiple values?

That is the focus of Experiment 13.

Here we replace our slide switches from Ex12 with a 10-bit binary counter, and connect our ROM data output to **spi2dac** and **pwm** modules.

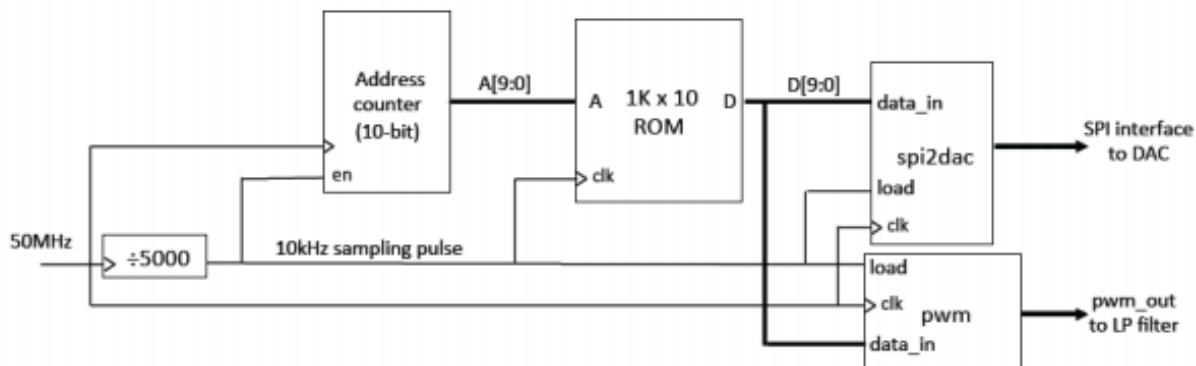The block diagram for this is as follows:



We implemented the circuit design specified in the schematic above as follows:

The code works as follows:

TOP FUNCTION:

```
4   output DAC_CS;
5   output DAC_SDI;
6   output DAC_LD;
7   output DAC_SCK;
8   output PWM_OUT;
```

```

9
10    wire tick, load;
11    wire [9:0] A;
12    wire [9:0] D;
13
14
15    clkTick_16 TICK(CLOCK_50, tick);
16    assign Load = tick;
17
18    reg reset_count;
19    initial reset_count = 1'b0;
20    counter_16 COUNT(CLOCK_50, load, reset_count, A);
21
22    ROM rom(A, load, D);
23
24    spi2dac SPI2DAC(CLOCK_50, D, load, DAC_SDI, DAC_CS, DAC_SCK, DAC_LD);
25
26    pwm PWM(CLOCK_50, D, load, PWM_OUT);
27
28    always @ (posedge CLOCK_50)
29    begin
30        if (reset_count == 16'd1023)
31            reset_count <= 1'b1;
32        else
33            reset_count <= 1'b0;
34    end
35
36 endmodule
37

```

Two "utility" modules were added to the function.

- Address counter
- 10kHz sampling pulse

We added this 10-bit counter as follows:

```

1  `timescale 1ns / 100ps
2
3  module counter_16(
4      clock,
5      enable,
6      reset,
7      count
8  );
9
10 parameter BIT_SZ = 16;
11 input clock;
12 input enable;
13 input reset;
14 output [BIT_SZ-1:0] count;
15
16 reg [BIT_SZ-1:0] count;
17
18 initial count = 0;
19
20 always @ (posedge clock) begin
21     if (enable==1'b1 && reset==1'b0)
22         count <= count + 1'b1;
23     else if (enable==1'b1 && reset==1'b1)
24         count = 1'b0;
25


```

```
25      ena  
26  endmodule  
27
```

```
1  module clkdiv_16( //DIVIDE BY 500  
2  |  clkin,  
3  |  tick);  
4  
5  |  input clkin;  
6  |  output tick;  
7  
8  |  reg [13:0] count;  
9  |  reg tick;  
10  
11  
12  |  initial tick = 1'b0;  
13  |  initial count = 0;  
14  
15  |  always @ (posedge clkin)  
16  |  begin  
17  |  |  if (count == 3'd500)  
18  |  |  begin  
19  |  |  |  tick <= 1'b1;  
20  |  |  |  count <= 0;  
21  |  |  end  
22  |  |  else  
23  |  |  begin  
24  |  |  |  count <= count + 1'b1;  
25  |  |  |  tick <= 1'b0;  
26  |  |  end  
27  |  end  
28  
29  endmodule  
30
```

Having implemented these modules, we had to test whether it was indeed working.

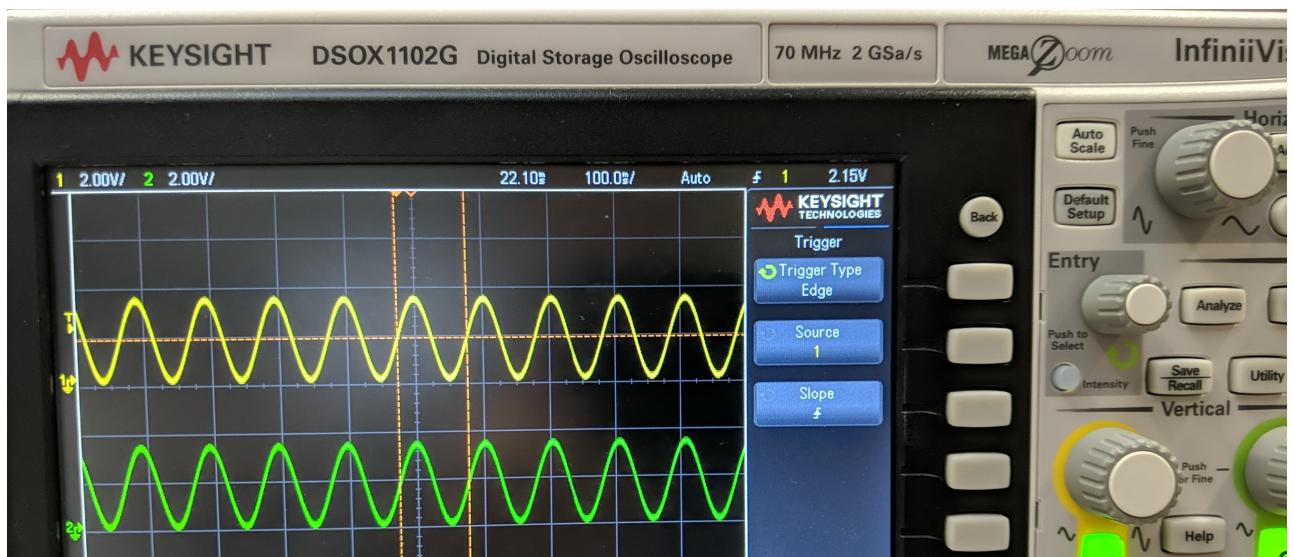Hence, we connected to TP8 and TP9, checking if it was giving the elusive sine wave we were looking for





The sine waves we received at TP8 and TP9 were the same, both holding peak to peak of 3.6V, and the following frequencies:

DAC signal – Frequency: 9.76Hz

PWM signal – Frequency: 9.76Hz

We received two key takeaways from this experiment:

1. Our DAC and PWM modules didn't work "by luck"- they were both genuinely capable of taking any digital value and converting it into analog, with good accuracy. This was shown with how they both interpreted at the same 9.76Hz, similar to peers in the lab.
2. **The frequency of the sinewave in our 1K x 10 ROM is shown to be 9.76Hz**

Experiment 14 (Optional): A variable sinewave generator

Sunday, December 8, 2019 1:55 PM


- Design a sinewave tone generator, with variable frequency, controlled by slide switches, and shown on 7-seg displays in decimal format

In Experiment 12, we learnt how to use switches to read from a ROM and output it on a 7-seg display.

In Experiment 13, we learnt how to count through a ROM using a counter, and output it onto two analogue outputs.

Here, we are tasked to combine these 2 lessons to create a variable sinewave generator.

The block diagram is as follows:

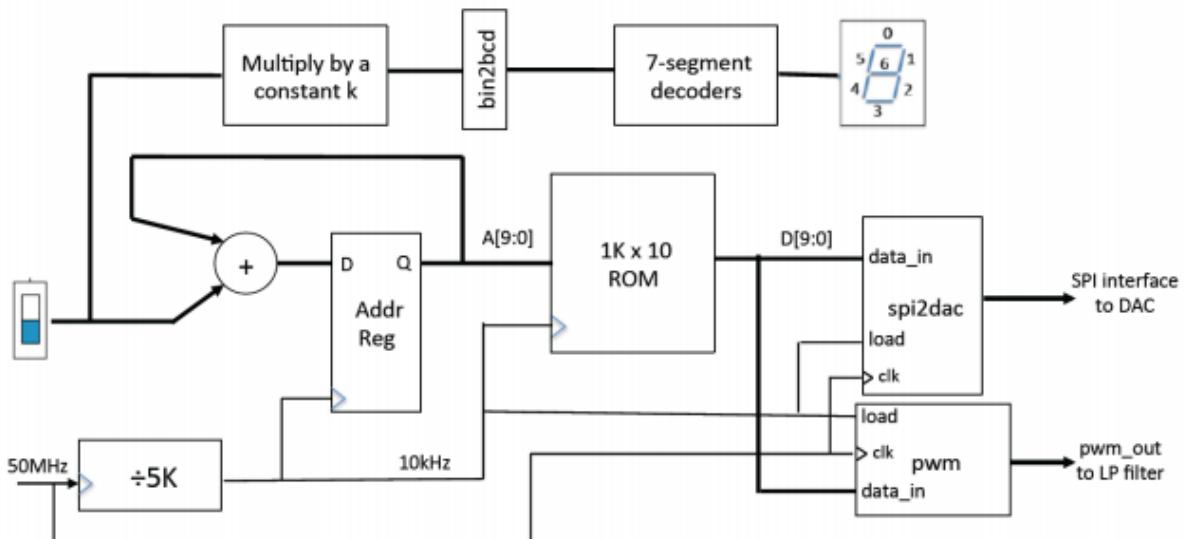

Lower part: understanding the frequency maneuver and modifying experiment 13

We immediately notice that we can reuse our bottom half (div5k, address counter, ROM, spi2dac, pwm) modules from experiment 14.

All we have to amend from it, is to add an adder block before the counter, adding our current address with the value in our switches SW[9:0].

Why? This allows us to "skip" values in our ROM at each iteration. For example, if our switches were set to 2, we would be reading **every 2** values in our ROM – while still at 10kHz. Hence, in this case we are doubling our frequency.

We can generalize this to any "skip" x is equivalent to a multiple of our function frequency.

Upper part: understanding the decimal multiplication and displaying necessary value

Whereas the bottom part is concerned with changing our output frequency, the top is simply in charge of displaying this change on a screen.

The first block of interest is **Multiply by a constant k** block. We can create this constant coefficient multiplier using the IP-catalog tool- but before doing so, we first need to decide on what exactly is our constant k !


If the bottom part is focused on multiplying the frequency of the sinewave in our ROM, and last experiment we established that this frequency was 9.76Hz, we know this is what we need to multiply by!


We tried doing this in our IP catalog, but couldn't input a decimal value as datab.

We realized we could only do integer operations, so had to be a little more inventive.

It was here that we realized the importance of the top-14 bits and exactly why we were encouraged to multiply by the 14-bit constant 14'h2710. Because by multiplying by 14'h2710 (which is 14'd1000) and then keeping the top 14 bits, we were essentially bit shifting our product 10 bits to the right- dividing it by 2^{10} .

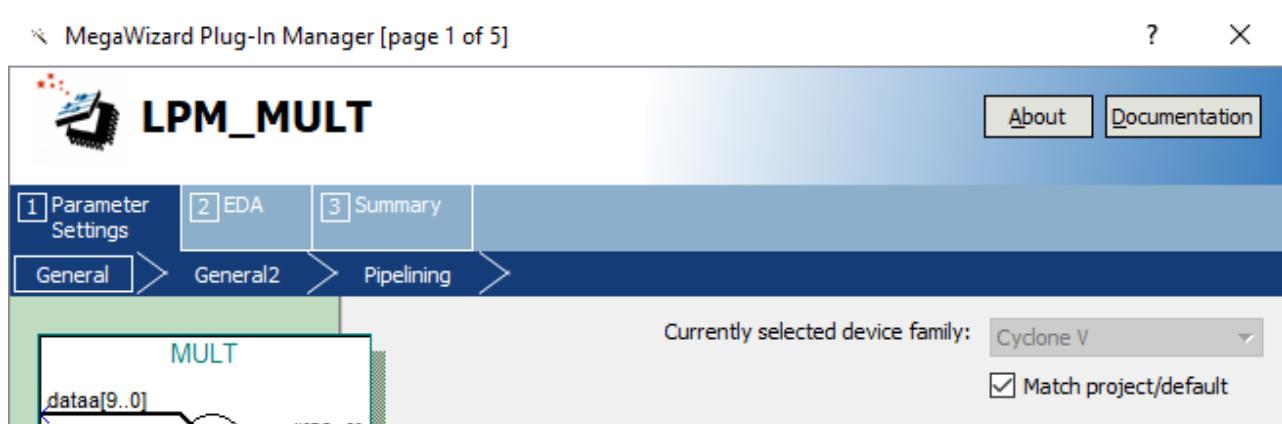$10000/(2^{10}) = 9.7656 \rightarrow$ the constant we were looking for!



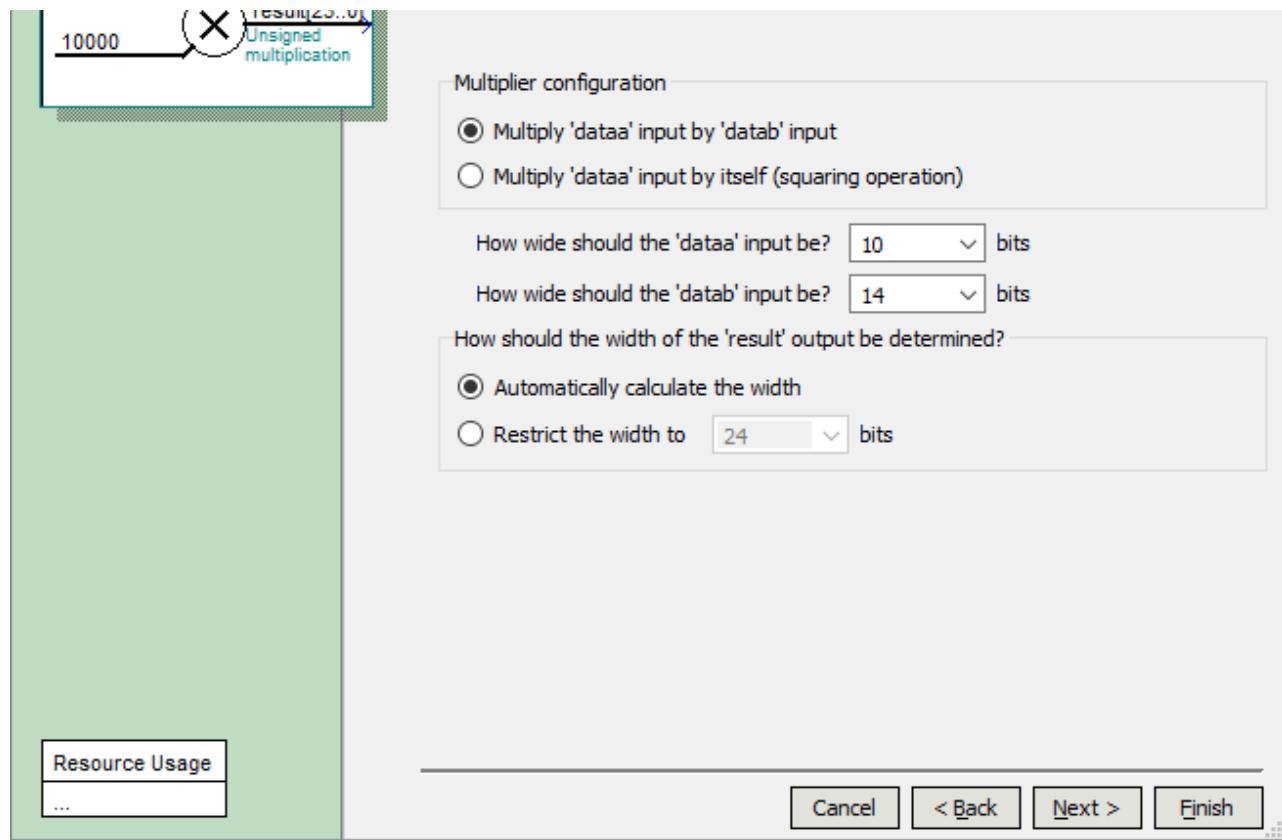

Selection of top 14 bits:

```
33     bin2bcd_16 top14_to_bcd({2'b0, MULT_RES[23:10]}), BCD0, BCD1, BCD2, BCD3, BCD4);
```

Top function:

```
1  module ex14_top(
2    CLOCK_50,
3    SW,
4    HEX0, HEX1, HEX2, HEX3, HEX4,
5    DAC_SDI, DAC_CS, DAC_SCK, DAC_LD,
6    PWM_OUT);
7
8    input CLOCK_50;
9    input [9:0] SW;
10
11   output [6:0] HEX0, HEX1, HEX2, HEX3, HEX4;
12   output DAC_SDI, DAC_CS, DAC_SCK, DAC_LD, PWM_OUT;
13
14   wire TICK_10KHZ;
15   wire [9:0] DATA;
16   wire [3:0] BCD0, BCD1, BCD2, BCD3, BCD4;
17   wire [23:0] MULT_RES;
18
19   reg [9:0] COUNT;
20
21   initial COUNT = 10'b0;
22
23   clk16_div_5k(CLOCK_50, TICK_10KHZ, 16'd5000, 1'b1);
24
25   ROM rom_data(COUNT, TICK_10KHZ, DATA);
26
27   spi2dac analogue_out0(CLOCK_50, DATA, TICK_10KHZ, DAC_SDI, DAC_CS, DA
28
29   pwm analogue_out1(CLOCK_50, DATA, TICK_10KHZ, PWM_OUT);
```

```
50
31    MULT times_10k(sw,MULT_RES);
32
33    bin2bcd_16 top14_to_bcd({2'b0, MULT_RES[23:10]}, BCD0, BCD1, BCD2, BC
34
35    hex_to_7seg SEG0(HEX0, BCD0);
36    hex_to_7seg SEG1(HEX1, BCD1);
37    hex_to_7seg SEG2(HEX2, BCD2);
38    hex_to_7seg SEG3(HEX3, BCD3);
39    hex_to_7seg SEG4(HEX4, BCD4);
40
41    always @ (posedge TICK_10KHz)
42        COUNT <= COUNT + sw;
43
44 endmodule
45
```

Experiment 15 (Optional Challenge): Using the A-to-D converter

Sunday, December 8, 2019

1:56 PM

Key outcome of experiment 15:


- Use the Analogue-to-Digital converter MCP3002 to convert dc voltages

At the beginning of part 3, we set out to do many things, such as understanding the SPI, using a ROM, and using an ADC to convert DC voltages.


We achieved all these goals except for the last. We felt this was a necessary challenge for us to understand the relation between both directional flows of digital and analogue data.

The task was clearcut- "instead of using the slide switches to control the frequency, use the DC voltage of the potentiometer (which is between 0v and 3.3v) and use this converted

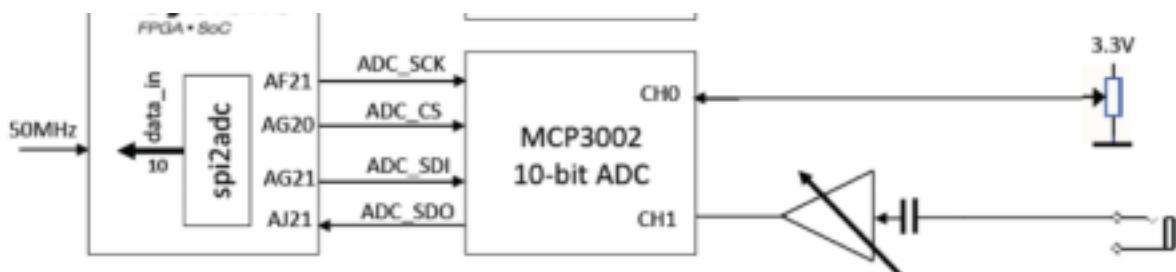We weren't sure about the potentiometer component, so referred to our board schematic.




Once we familiarized ourselves with the voltage source/potentiometer as shown in the diagram, we realized that this experiment was a clone copy of experiment 14, except with our analogue potentiometer instead of the switches we were familiar with.

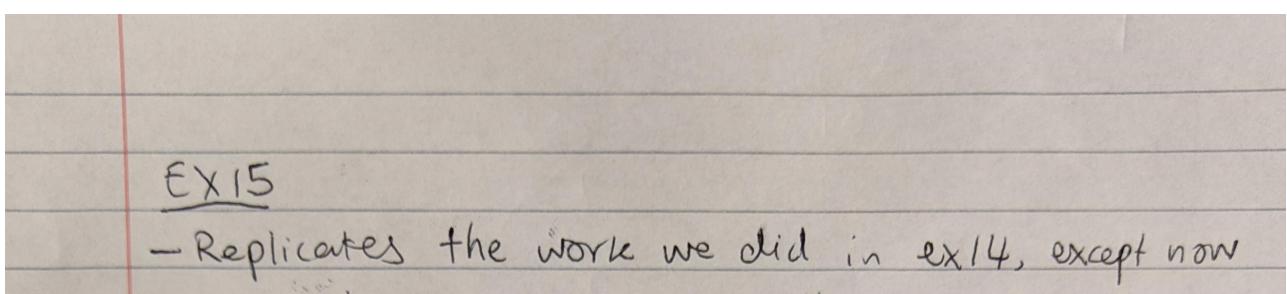

EX15

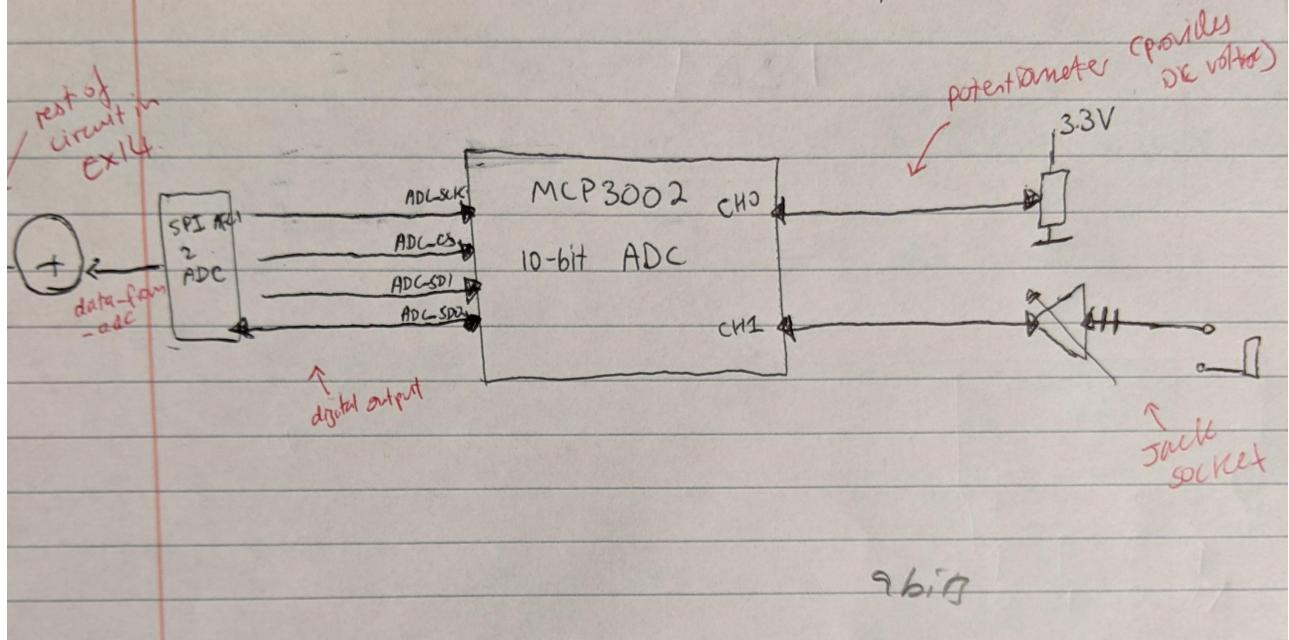— Replicates the work we did in ex14, except now we replace our switches with the potentiometer.



To work with this analogue source, we would have to include the spi2adc to turn these into bits we can work with in our circuit. The adder is the "plug" to what we completed in experiment 14.

We implemented this as follows:

```

1  module ex15_top(
2    CLOCK_50,
3    HEX0, HEX1, HEX2, HEX3, HEX4,
4    DAC_SDI, DAC_CS, DAC_SCK, DAC_LD,
5    ADC_SDI, ADC_CS, ADC_SCK, ADC_SDO,
6    PWM_OUT);
7
8  parameter channel = 1'b0;
9
10 input CLOCK_50;
11 input ADC_SDO;
12
13 output ADC_CS, ADC_SCK, ADC_SDI;
14 output [6:0] HEX0, HEX1, HEX2, HEX3, HEX4;
15 output DAC_SDI, DAC_CS, DAC_SCK, DAC_LD, PWM_OUT;
16
17
18 wire TICK_10KHz;
19 wire [9:0] DATA;
20 wire [9:0] a2d_data;
21 wire [3:0] BCD0, BCD1, BCD2, BCD3, BCD4;
22 wire [23:0] MULT_RES;
23
24 reg [9:0] COUNT;
25
26 initial COUNT = 10'b0;
27
28 clk_tick_16 div_5k(CLOCK_50, TICK_10KHz, 16'd5000, 1'b1);
29
30 ROM rom_data(COUNT, TICK_10KHz, DATA);
31
32 spi2dac analogue out0(clock_50, DATA, TICK_10KHz, DAC_SDO, DAC_CS, DAC_SCK, DAC_LD);

```

```

33
34     spi2adc analogue_in(
35         .sysclk (CLOCK_50),
36         .channel (1'b0),
37         .start (TICK_10KHz),
38         .data_from_adc (a2d_data),
39         .data_valid (data_valid),
40         .sdata_to_adc (ADC_SDI),
41         .adc_cs (ADC_CS),
42         .adc_sck (ADC_SCK),
43         .sdata_from_adc (ADC_SDO));
44
45     pwm analogue_out1(CLOCK_50, DATA, TICK_10KHz, PWM_OUT);
46
47     mult_24 times_10k(DATA,MULT_RES);
48
49     bin2bcd_16 top14_to_bcd({2'b0, MULT_RES[23:10]}, BCD0, BCD1, BCD2, BCD3, BCD4);
50
51     hex_to_7seg SEGO(HEX0, BCD0);

```

From the code, we note the implementation of spi2adc. We are passing signals tick_10k as the load input, and have selected channel 0 for the SPI-ADC input (so that we may read from our potentiometer).

A2data is our address offset to be added to our counter. This is done at the very end of our top function, as follows:

```

57     always @ (posedge TICK_10KHz)
58         COUNT <= COUNT + a2d_data;
59

```

Successfully extending Exp.14 for analogue input.

SPI2ADC

```

7 //-----
8
9 module spi2adc (sysclk, start, channel, data_from_adc, data_valid,
10   sdata_to_adc, adc_cs, adc_sck, sdata_from_adc);
11
12   input sysclk;           // 50MHz system clock of DE0
13   input start;            // Pulse to start ADC, minimum wide = clock period
14   input channel;          // channel 0 or 1 to be converted
15   output [9:0] data_from_adc; // 10-bit ADC result
16   output data_valid;      // High indicates that converted data valid
17   output sdata_to_adc;    // Serial commands send to adc chip
18   output adc_cs;          // chip select - low when converting
19   output adc_sck;         // SPI clock - active during conversion
20   input sdata_from_adc;   // Converted serial data from ADC, MSB first
21
22 //-----Input Ports-----
23 // All the input ports should be wires
24 wire sysclk, start, sdata_from_adc;
25
26 //-----Output Ports-----
27 // output port can be a storage element (reg) or a wire
28 reg [9:0] data_from_adc;
29 reg adc_cs;
30 wire sdata_to_adc, adc_sck, data_valid;
31
32 //-----Configuration parameters for ADC -----
33 parameter SGL=1'b1; // 0:diff i/p, 1:single-ended
34 parameter MSBF=1'b1; // 0:LSB first, 1:MSB first
35
36 // --- Submodule: Generate internal clock at 1 MHz ---
37 reg clk_1MHz; // 1MHz clock derived from 50MHz
38 reg [4:0] ctr; // internal counter
39 reg tick; // 1MHz clock tick lasting 20ns, i.e. one 50MHz cycle
40 parameter TIME_CONSTANT = 5'd24; // change this for diff clk freq
41
42 initial begin
43   clk_1MHz = 0; // don't need to reset - don't care if it is 1 or 0 to start
44   ctr = 5'b0; // ... to start. Initialise to make simulation easier
45   tick = 1'b0;
46 end
47
48 always @ (posedge sysclk) //
49   if (ctr==0) begin
50     ctr <= TIME_CONSTANT;
51     if (clk_1MHz==1'b0)
52       tick <= 1'b1;
53     clk_1MHz <= ~clk_1MHz; // toggle the output clock for squarewave
54   end
55 else begin
56   ctr <= ctr - 1'b1;

```

```


56     tick <= 1'b0;
57   end
58 // ---- end internal clock generator -----
59 // ---- Detect start is asserted with a small state machine
60
61
62
151
      tick <= 1'b0;
    end
  // ---- end internal clock generator -----
  // ---- Detect start is asserted with a small state machine
  // .... FF set on positive edge of start
  // .... reset when adc_cs goes high again
  reg [1:0] sr_state;
  parameter IDLE = 2'b00, WAIT_CSB_FALL = 2'b01, WAIT_CSB_HIGH = 2'b10;
  reg adc_start;
  initial begin
    sr_state = IDLE;
    adc_start = 1'b0; // set while sending data to ADC
  end
  always @ (posedge sysclk)
    case (sr_state)
      IDLE: if (start==1'b0) sr_state <= IDLE;
      else begin
        sr_state <= WAIT_CSB_FALL;
        adc_start <= 1'b1;
      end
      WAIT_CSB_FALL: if (adc_cs==1'b1) sr_state <= WAIT_CSB_FALL;
      else sr_state <= WAIT_CSB_HIGH;
      WAIT_CSB_HIGH: if (adc_cs==1'b0) sr_state <= WAIT_CSB_HIGH;
      else begin
        sr_state <= IDLE;
        adc_start <= 1'b0;
      end
      default: sr_state <= IDLE;
    endcase
  //----- End circuit to detect start and end of conversion
  // spi controller designed as a state machine
  // .... with 16 states (idle, and S1-S15 indicated by state value
  reg [4:0] state;
  reg adc_done, adc_din, shift_ena;
  initial begin
    state = 5'b0; adc_cs = 1'b1; adc_done = 1'b0;
    adc_din = 1'b0; shift_ena <= 1'b0;
  end
  always @(posedge sysclk)
    if (tick==1'b1) begin
      // default outputs and state transition
      adc_cs <= 1'b0; adc_done <= 1'b0; adc_din <= 1'b0; shift_ena <= 1'b0;
      state <= state + 1'b1;
      case (state)
        5'd0: begin
          if (adc_start==1'b0) begin
            if (tick==1'b1) begin
              // default outputs and state transition
              adc_cs <= 1'b0; adc_done <= 1'b0; adc_din <= 1'b0; shift_ena <= 1'b0;
              state <= state + 1'b1;
              case (state)
                5'd0: begin
                  if (adc_start==1'b0) begin
                    state <= 5'd0; // still idle
                    adc_cs <= 1'b1; // chip select not active
                  end
                  else begin
                    state <= 5'd1; // start converting
                    adc_din <= 1'b1; // start bit is 1
                  end
                end
                5'd1: adc_din <= SGL; // SGL bit
                5'd2: adc_din <= channel; // CH bit
                5'd3: adc_din <= MSBF; // MSB first bit
                5'd4: shift_ena <= 1'b1; // start shifting data from adc
                5'd15: begin
                  shift_ena <= 1'b0;
                  adc_done <= 1'b1;
                end
                5'd16: begin
                  adc_cs <= 1'b1; // last state - disable chip select
                  state <= 5'd0; // go back to idle state
                end
                default:
                  shift_ena <= 1'b1; // unspecified states are covered by default above
              endcase
            end
          end
        end
      // ... always
      // shift register for output data
      reg [9:0] shift_reg;
      initial begin
        shift_reg = 10'b0;
        data_from_adc = 10'b0;
      end
      always @(negedge sysclk)
        if((adc_cs==1'b0)&&(shift_ena==1'b1)&&(tick==1'b1)) // start shifting data_in
          shift_reg <= {shift_reg[8:0],sdata_from_adc};
      // Latch converted output data
      always @(posedge sysclk)
        if(adc_done)
          data_from_adc = shift_req;
    end

```

Experiment 16: An audio in-and-out (all pass) loop

Sunday, December 8, 2019 1:56 PM

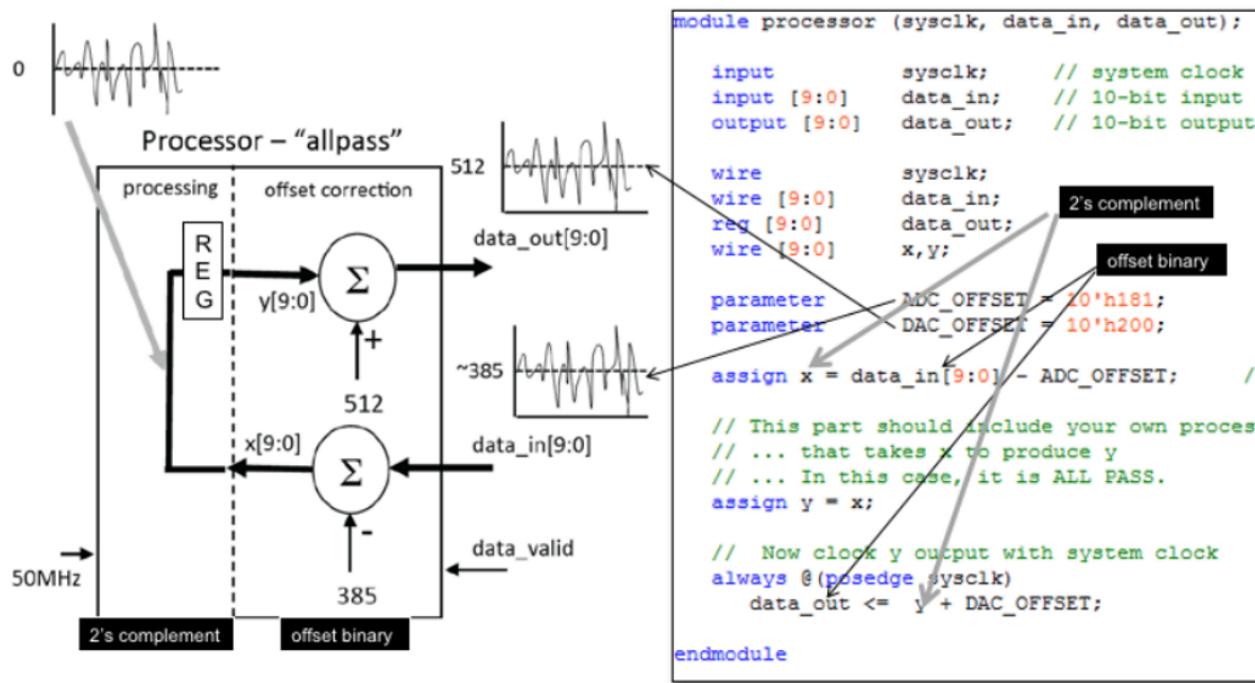In Experiment 16, we were tasked with understanding the ALLPASS processing module. The code for which is analyzed below:



The input `data_in[9:0]` is used to represent the analogue signal input (which is bipolar) as offset binary. There is an offset of ~ 385 if the input is connected to 0 (no signal) - the output `data_out[9:0]` also has an offset. To get $V_{out} = 0V$, you need to send in the binary number 512.

To process the signal using normal arithmetic operations such as `+` or `*` we need to use the 2s compliment number system so that the ADC data is offset correctly by subtracting the 385 from the converted data to yield `x[9:0]`. Then the output `y[9:0]` is again converted back to offset binary for the DAC to output it. This is done by adding 512 to `y[9:0]`.

We were also tasked with creating a `mult4` module which amplifies the input signal by 4 before outputting it. This was achievable by performing an arithmetic shift left by 2 bits.

```
module mult4(
    data_in,
```

```

data_out)

input [9:0] in;
output [9:0] out;

assign data_out[9:0] = {data_in [7:0], 2'b0}; //Logical shift by 2 (i.e. multiply by 4)
endmodule

module ex16_top (CLOCK_50, SW, HEX0, HEX1, HEX2,
                  DAC_SDI, DAC_SCK, DAC_CS, DAC_LD,
                  ADC_SDI, ADC_SCK, ADC_CS, ADC_SDO, PWM_OUT);

    input      CLOCK_50;           // DE0 50MHz system clock
    input [9:0] SW;               // 10 slide switches to specify address to ROM
    output [6:0] HEX0, HEX1, HEX2;
    output     DAC_SDI;           //Serial data out to SDI of the DAC
    output     DAC_SCK;           //Serial clock signal to both DAC and ADC
    output     DAC_CS;            //chip select to the DAC, low active
    output     DAC_LD;            //Load new data to DAC, low active
    output     ADC_SDI;           //Serial data out to SDI of the ADC
    output     ADC_SCK;           // ADC clock signal
    output     ADC_CS;            //chip select to the ADC, low active
    input      ADC_SDO;           //Converted serial data from ADC
    output    PWM_OUT;            // PWM output to R channel

    wire      tick_10k;           // internal clock at 10kHz
    wire [9:0] data_in;           // converted data from ADC
    wire [9:0] data_out;          // processed data to DAC
    wire      data_valid;
    wire      DAC_SCK, ADC_SCK;

    clk1k GEN_10K (CLOCK_50, 1'b1, 16'd4999, tick_10k); // generate 10KHz
    spi2dac SPI_DAC (CLOCK_50, data_out, tick_10k,           // send processed sample to DAC
                      DAC_SDI, DAC_CS, DAC_SCK, DAC_LD); // order of signals matter
    pwm PWM_DC(CLOCK_50, data_out, tick_10k, PWM_OUT); // output via PWM - R-channel

    spi2adc SPI_ADC (
        .sysclk (CLOCK_50),
        .channel (1'b1), // perform a A-to-D conversion
        .start (tick_10k), // order of parameters do not matter
        .data_from_adc (data_in),
        .data_valid (data_valid),
        .sdata_to_adc (ADC_SDI),
        .adc_cs (ADC_CS),
        .adc_sck (ADC_SCK),
        .sdata_from_adc (ADC_SDO));
    processor ALLPASS (CLOCK_50, data_in, data_out); // do some processing on data

    hex_to_7seg SEG0 (HEX0, data_in[3:0]);
    hex_to_7seg SEG1 (HEX1, data_in[7:4]);
    hex_to_7seg SEG2 (HEX2, {2'b0,data_in[9:8]});

endmodule

```

```

module processor (sysclk, data_in, data_out);

    input      sysclk;           // system clock
    input [9:0] data_in;          // 10-bit input data
    output [9:0] data_out;         // 10-bit output data

    wire      sysclk;
    wire [9:0] data_in;

```

```
reg [9:0]      data_out;
wire [9:0]      x,y;

parameter      ADC_OFFSET = 10'h181;
parameter      DAC_OFFSET = 10'h200;

assign x = data_in[9:0] - ADC_OFFSET;      // x is input in 2's complement
// This part should include your own processing hardware
// ... that takes x to produce y
// ... In this case, it is ALL PASS.
assign y = x;

// Now clock y output with system clock
always @(posedge sysclk)
  data_out <= y + DAC_OFFSET;

endmodule
```